



TurbolEG.com



اسئلة مقترحة :

مختبر الالكترونيات و الآلات الكهربائية

Electro Machine Lab

اللجنة الأكاديمية لقسم الهندسة الصناعية

2023



# Electronics Lab

## Questions

Questions link:

<https://forms.gle/v8ETK2tnVKRX5dzV8>

**Solve the answers below**

# Question No.1

1-The main difference between clipper and clamper is the presence of:

**Capacitor**

2-The transistor has  $V_c=4V$  , $V_b=3V$  and  $V_e=5V$  , then the transistor is biased in

$V_b < V_c$  Reverse

$V_b < V_e$  Reverse

**Cut off mode**

3- The term BJT is short for

**bipolar junction transistor**

4- Compared to HWR,the FWR has

Full wave Rectifier has:

low ripple voltage= $V_P/2R_{FC} = 1/2 * (\text{low ripple voltage half wave})$

**low ripple voltage**

5- A certain transistor has  $I_C = 15 \text{ mA}$  and  $I_B = 167 \mu\text{A}$ ; DC is

$\beta = I_C/I_B = 15\text{mA}/167 \mu\text{A} =$

**90**

6- is an electronic circuit that changes the DC level of a signal to the desired level without changing the shape of the applied signal

**Clamper**

7- The circuit which changes the shape of AC input signal is called

**Clipper**

8- The transistor has  $V_c=2V$  , $V_b=3V$  and  $V_e=1V$  , then the transistor is biased in

$V_b > V_c$  Forward

$V_b > V_e$  Forward

**Saturation mode**

9-  $I_d=3\text{mA}$  ,  $V_d=0.66\text{V}$  and when  $I_d=3.5\text{mA}$  ,  $V_d=0.7\text{V}$ , the Dynamic or AC Resistance  $r_{ac} =$


$$= \Delta V / \Delta I$$

$$= 0.7 - 0.66 / 3.5 \text{ mA} - 3 \text{ mA} =$$

**80  $\Omega$**

10- Which of the following diodes is reverse biased

Forward Biased

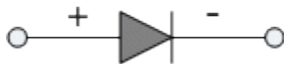

Reversed Biased



**A**

11-What are the two types of bipolar junction transistors

**npn and pnp**

12- The transistor has  $V_c=4\text{V}$  ,  $V_b=3\text{V}$  and  $V_e=1\text{V}$  , then the transistor is biased in


$V_b < V_c$  Reverse

$V_b > V_e$  Forward

**Forward Active mode**

13- In which of the following figures, junction diode is forward biased

Forward Biased

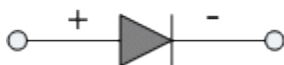

Reversed Biased



**B**

## Question No.2

1- For the circuit shown below consider  $V_Y=0.6$  then fill the table

D  $V_Y = 0.6$

$V_Y > V_S$	$V_Y < V_S$	$V_Y = V_S$
$V_Y > V_S \rightarrow$	$V_Y < V_S \rightarrow$	$V_Y = V_S \rightarrow$
$V_Y > V_S \rightarrow$	$V_Y < V_S \rightarrow$	$V_Y = V_S \rightarrow$
$V_Y < V_S \rightarrow$	$V_Y < V_S \rightarrow$	$V_Y = V_S \rightarrow$
$V_Y < V_S \rightarrow$	$V_Y < V_S \rightarrow$	$V_Y = V_S \rightarrow$
$V_Y < V_S \rightarrow$	$V_Y < V_S \rightarrow$	$V_Y = V_S \rightarrow$

Note:-  
 $V_Y > V_S = V_S$   
 $V_Y < V_S = V_Y$   
 $V_Y = V_S = V_S$

KVL:-

- $-0.2 + 0.2 + V_R = 0 \rightarrow V_R = 0$
- $-0.5 + 0.5 + V_R = 0 \rightarrow V_R = 0$
- $-0.9 + 0.6 + V_R = 0 \rightarrow V_R = 0.3$
- $-1 + 0.6 + V_R = 0 \rightarrow V_R = 0.4$
- $-3 + 0.6 + V_R = 0 \rightarrow V_R = 2.4$

$V_R$
0
0
0.3
0.4
2.4

IF  $= \frac{V_R}{R} = \frac{0}{1k\Omega} = 0$

IF  $= \frac{V_R}{R} = \frac{0.3}{1} = 0.3mA$

IF
0
0
0.3
0.4
2.4

2) the RD at 3V

$$RD = VD/IF = 0.6/2.4 \times 10^{-3} = 250$$

3) the rD at 1V

$$rD = \Delta V / \Delta i = VD(3) - VD(0.9) / IF(3) - IF(0.9) = 0.6 - 0.6 / 2.4 - 3 = 0$$

## Question No.3

1) For the circuit shown below ,the  $V_o$  Avg is

$$V_P - V_Y / \pi =$$

$$5 - 0.6 / \pi = 1.4$$

2) For the circuit the average power dissipated in the diode is

$$V = IR$$

$$0.6 = I * 2000$$

$$I = 0.3 \text{mA}$$

$$P = VI$$

$$P = 1.4 * 0.3 \text{Ma} = 0.42 \text{mW}$$


## Question No.4

1) For the circuit shown below , What is the name of the circuit

Clipper

2) the output wave form ( $V_D=0.7$ )

A

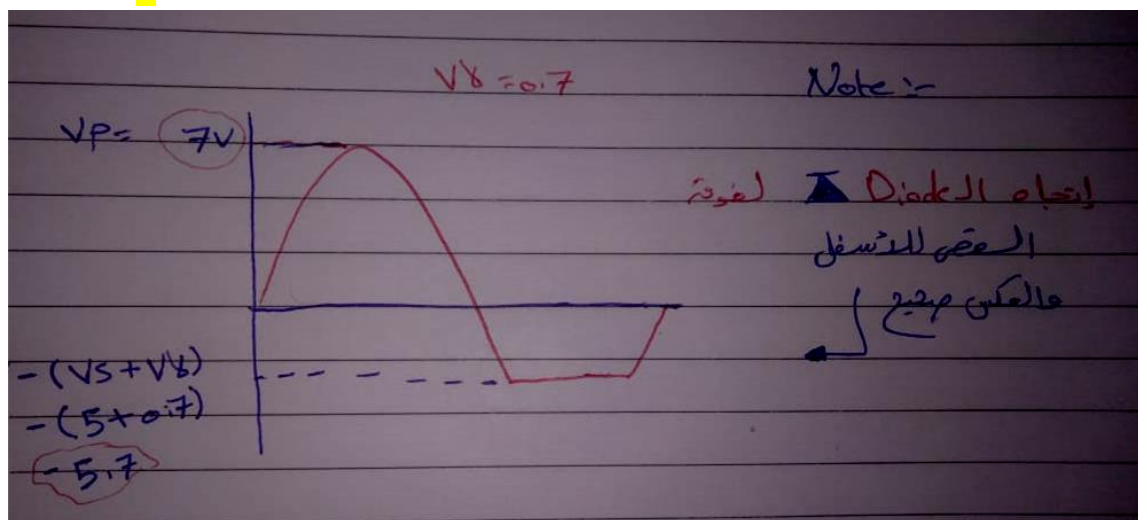

## Question No.5

$$1) \underline{I_B} = \frac{V_{BB} - V_{BE(on)}}{R_B} = \frac{5 - 0.6}{100k\Omega} = 0.044mA$$

$$2) \underline{I_C} = \beta I_B = 100 * 0.044 \times 10^{-3} = 4.4mA$$

$$3) \underline{I_E} = I_C + I_B = 0.044 + 4.4 = 4.444mA$$

$$4) V_{CE} \rightarrow$$

$$V_{CC} = I_C * (R_C + R_E) + V_{CE}$$

$$10 = 4.4 \times 10^{-3} (2 \times 10^3 + 0) + V_{CE}$$

$$\underline{V_{CE} = 1.2V}$$




## Question No.6

1) For the circuit shown below , What is the name of the circuit ? (Ideal diode)

Clamper

2) the output wave form

c

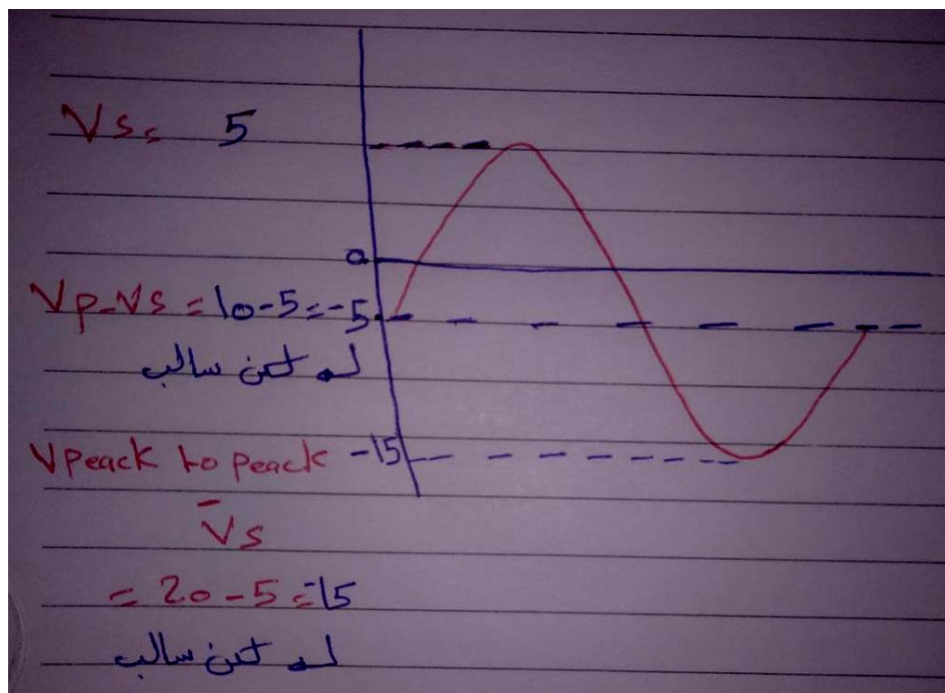

## Question No.7

1) For the circuit shown below (Ideal diode), the circuit represents

full wave rectifier

2) The average value of the output signal is


$$= 2V_{inp} / \pi$$

$$2 \times 5 / \pi$$

$$= 3.18\text{v}$$

3) the output wave form

B

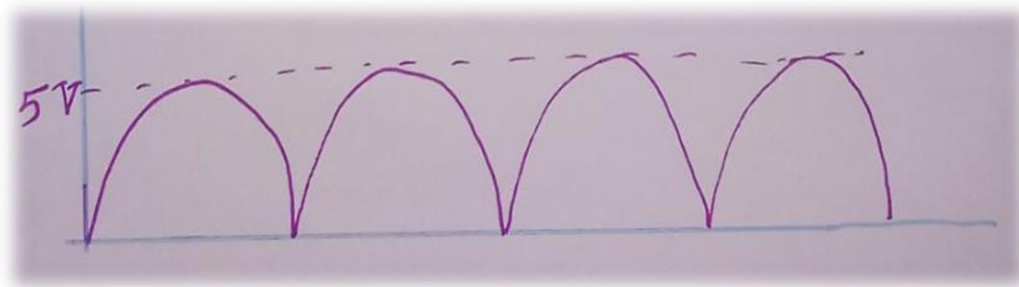

# Question No.8

1) For the following circuit below fill the table below

**B**

KVL:-

$V_8 \leq 0.7$

$V_{out}$
0
0
0.1
0.3

$\rightarrow -0.3 + 0.3 + V_{out} = 0 \Rightarrow V_{out} = 0$

VD 11 do  
Vout 10.3

VD
0.3
0.4
0.7
0.7

$V_8 \leq 0.7$

Note:-

$V_8 > V_{in} = V_{in}$   
 $V_8 < V_{in} = V_8$   
 $V = V_{in} = V_{in}$


## Question No.9

1) For the circuit shown below assume (Ideal diode), the circuit represents

half wave rectifier

2) the output wave form

A

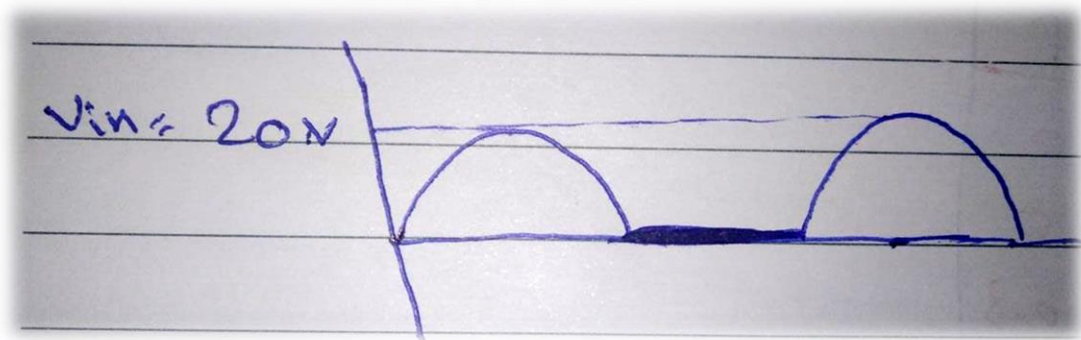

3) The average voltage

$$V_0 \text{ avg} = V_{in} / \pi$$


$$20 / \pi = 6.366 \text{ V}$$

4) The average current in the diode

$$I_d \text{ avg} = V_0 \text{ avg} / R_{\text{load}}$$

$$6.366 / 1000 = 6.36 \text{ mA}$$


## Question No.10

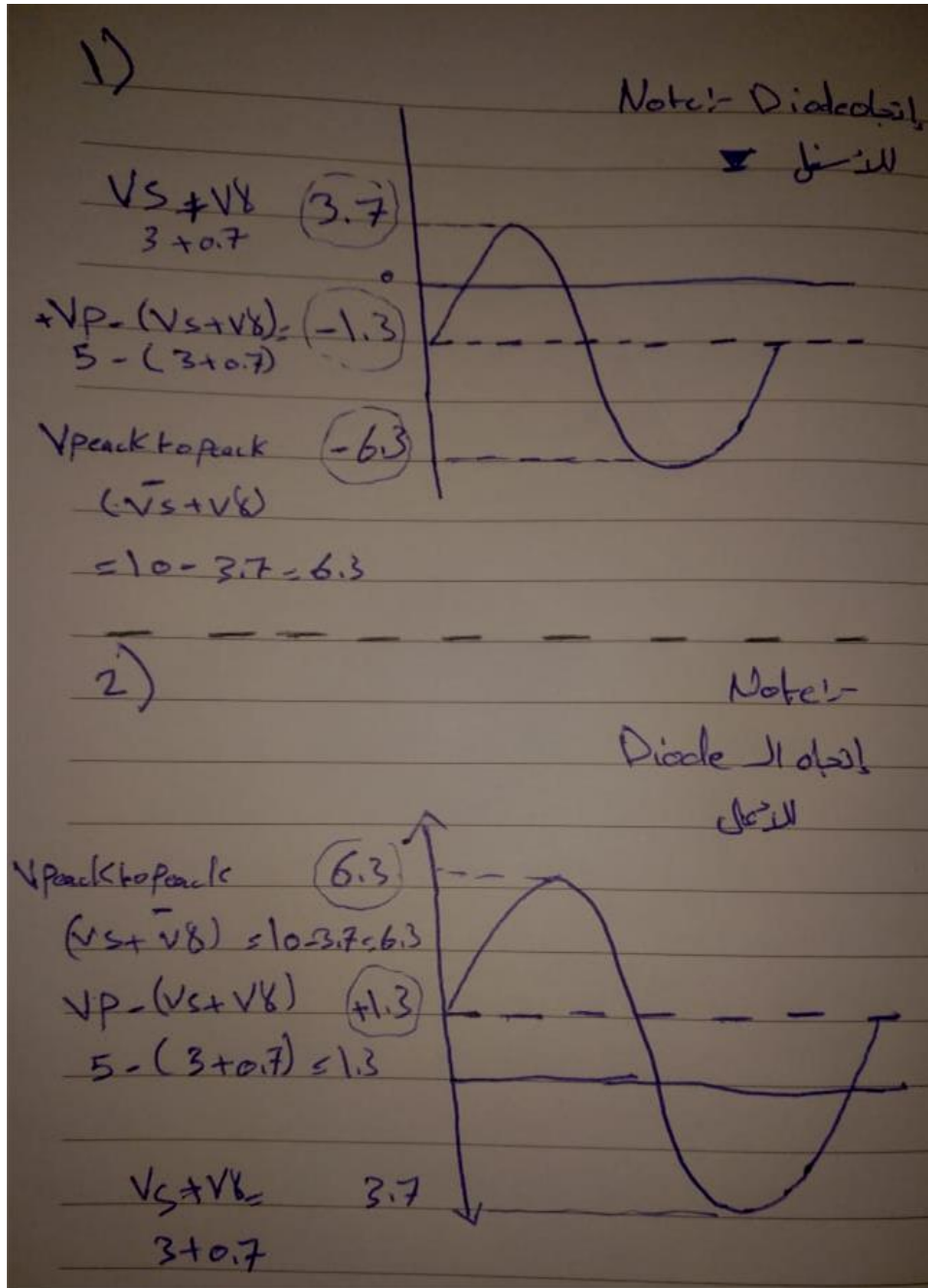

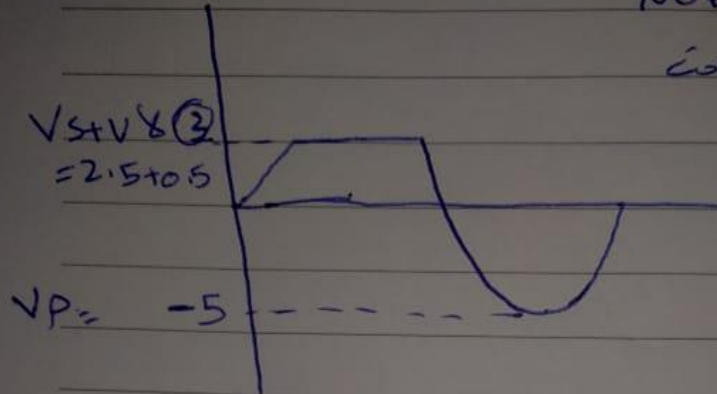3)

Note:


إتجاه الـ  $\nabla$  لتيمة  
التيمة لتيمة



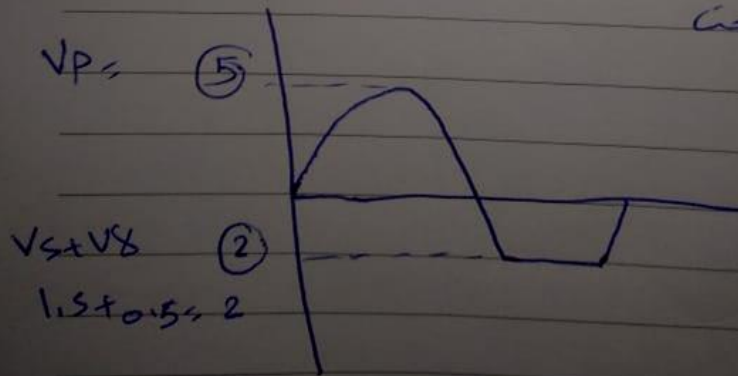4)

Note:

إتجاه الـ  $\nabla$  لتيمة  
التيمة لتيمة



# Question No.11

1) If  $\beta=200$  ,  $\alpha$  equal=

$$\alpha = \beta / 1 + \beta$$

$$200 / 1 + 200 = 65.66$$

2) If  $\alpha=0.99$  ,  $\beta$  equal=

$$\beta = \alpha / 1 - \alpha$$

$$0.99 / 1 - 0.99 = 99$$

3) If  $\beta=100$  and  $I_c=30\text{mA}$  ,  $I_B$  equal

$$I_B = I_c / \beta$$

$$30\text{mA} / 100 = 300 \mu\text{A}$$

# Question No.12

1) V Average in full wave formula

$$V_{\text{Average}} = 2(V_P - 2V_\gamma)/\pi$$

2) V Average in half wave (Ideal diode)

$$V_{\text{Average}} = V_P/\pi$$

3) V Average in half wave (offset diode) formula

$$V_{\text{Average}} = (V_P - V_\gamma)/\pi$$



## Question No.13

$$\begin{aligned} 1) V_{BB} \text{ or } V_{Th} &= \frac{R_1}{R_1 + R_2} * V_{CC} \\ &= \frac{10}{60} * 20 = 3.33 \text{ V} \end{aligned}$$

$$2) R_{Th} \text{ or } R_{Th} = \frac{R_1 \times R_2}{R_1 + R_2} = \frac{50 \times 10}{50 + 10} = 8.33 \text{ K}\Omega$$

$$\begin{aligned} 3) I_B &= \frac{V_{BB} - V_{BE(on)}}{R_B + (B+1) * R_E} \\ &= \frac{3.33 - 0.7}{\frac{10^3}{10} \times 8.33 + (200+1) * 1000} = 12.56 \text{ }\mu\text{A} \end{aligned}$$

$$4) I_C = \beta * I_B = 200 * 12.56 \text{ }\mu\text{A} = 2.513 \text{ mA}$$

$$5) I_E = (1 + \beta) * I_B = (1 + 200) * 12.56 \times 10^{-6} = 2.52 \text{ mA}$$

$$\begin{aligned} 6) V_{CE} &= V_{CC} - I_C (R_C + R_E) \\ &= 20 - 2.513 \times 10^{-3} (3000 + 1000) \\ &= 9.948 \text{ V} \end{aligned}$$

# Question No.14

1) What type of diode circuit is used to add or restore a dc level to an electrical signal

**Clamper**

2) An open circuit can have any voltage across its terminals, but the current is always

**0A**

3) Refer to the figure given below. Which diode arrangement will supply a negative output voltage?

**c**

4) What best describes the circuit

**Half-wave rectifier**

5) Which diode arrangement will supply a positive output voltage

**A**

6) When a transistor is used as a switch, it is stable in which two distinct regions

**saturation and cutoff**

7) Which of the following is true for an npn or pnp transistor

**$I_E = I_B + I_C$**

8) DC power should be connected to forward bias a diode as follows

**+anode, – cathode**

9) The average value of a half-wave rectified voltage with a peak value of 200V is

**$V_{\text{Average}} = V_P / \pi$**

**$= 200 / \pi = 63.7$**

10) bridge rectifier consists of

**4 diodes**

11) Which of the following is not a necessary component in a clamper circuit

**Independent DC Supply**

Diode, Capacitor and Resistor are necessary to build a clamper circuit. An independent DC supply is required to bring an additional shift

12) For a sinusoidal input of 20 V<sub>peak</sub> to the given circuit, what is the peak value of the output waveform

**25V**

Explanation: In the given circuit, the output becomes zero for  $v_i$  less than -5 V. Hence, the peak value of the output is 25 V owing to the additive effect of V for  $v_i$ .

13) For the given circuit for a 20 V<sub>peak</sub> sinusoidal input  $v_i$ , what is the value of  $v_i$  at which the clipping begins

**-5V**

Explanation: Considering the connection of diode, it is evident that the diode becomes reverse biased when  $v_i < -5$  V. Hence, clipping starts at -5 V.

14) The transistor has  $V_c=3V$ ,  $V_b=4V$  and  $V_e=5V$ , then the transistor is biased in

$V_b > V_c$  Forward

$V_b < V_e$  Reverse

**Reverse active mode**

15) What is the peak-to-peak voltage value (V<sub>PP</sub>)

$+10V - (-10V) = 20V$

16) is the conversion of alternating current (AC) to direct current (DC)

**Rectifier**

17) The basic rectifier circuits are

**A+B+C**

18) choose the correct answer

**A (NPN) - B (PNP)**

## Question No.15

1) For normal operation of a pnp BJT, the base must be \_\_\_\_\_ with respect to the emitter and \_\_\_\_\_ with respect to the collector

negative, positive

2)  $\beta_{DC}$  is the ratio of  $I_C$  to  $I_E$

False

3) Refer to this figure. Determine the minimum value of  $I_B$  that will produce saturation. Use  $V_{CE} = 0.2V$

Apply kirchoff's voltage law in the output side

$$10 = 4.7 \times 10^3 I_C + 0.2$$

on solving  $I_C = 2.085 \text{ ma.}$

For common emitter configuration we know  $I_C = \beta I_B$   
where  $\beta = 200$

$$\text{So, } I_B = 2.085 / 200 = 10.425 \mu A$$

4) In this circuit  $\beta_{DC} = 100$  and  $V_{IN} = 8 \text{ V}$ . The value of  $R_B$  that will produce saturation is: ( $V_{CE} = 0.2 \text{ v}$ ) ( $V_{BE} = 0.7 \text{ v}$ )

Then apply kcl for output circuit.

$$20 - 0.2 / 2.5 = 7.92 \text{ mA} = I_C$$

$$I_C = \beta I_B$$

$$I_B = I_C / \beta = 7.92 / 100 = 0.0792.$$

Then kvl for input side.

$$8 - 0.7 - 0.0792 \times R_B = 0,$$

$$R_B = (8 - 0.7) / 0.0792 = 92 \text{ kohms}$$

# Question No.16

1) Choose the correct answer below

A	function generator
B	capacitor
C	breadboard
D	digital multimeter
E	resistor
F	transistor
G	dual trace oscilloscope

2) These lines of five holes are known as

**nodes**

3) ripple voltage of half wave rectifier formula

$$V_r = (V_P - V_Y) / F * R * C$$

4) ripple voltage of full wave rectifier formula

$$V_r = (V_P - 2V_Y) / 2 * F * R * C$$

5) choose the right answer

**V avg full wave > V avg half wave**

6) What is the peak voltage value

**10**

7) Transistor biasing represents ..... Conditions

**d.c**

8) Operating point represents

**Zero signal values of IC and VCE**

9) Total emitter current is

**IB + IC**

10) ripple factor of half wave rectifier formula

$$\%r = (V_r / V_{avg}) * 100\%$$

11) The ripple factor of a full-wave rectifier circuit compared to that of a half wave rectifier circuit without filter is

less than half that for a half-wave rectifier circuit

12) Shunting the ac component away from the load is the task of a

Filter

13) From the given I-V characteristics of a silicon diode, what is the approximate value of  $r_{av}$  between marked points

Explanation:  $r_{av}$  is the average AC resistance, found between two marked points in the I-V graph. Here  $r_{av} = 0.1/14\text{mA} = 7\Omega$ .

14) What is the name of the figure below

zener diode

15) In the image below, the diode characteristics diagram Answer the questions below

A	reverse
B	forward