



ملاحظات :

مبادئ الآلات الكهربائية

Electric Machinery Fundamentals

زهرة غانم

للدكتورة

اللجنة الأكاديمية لقسم الهندسة الصناعية


2025



Turbo IEG.Com



Turbo Team Youtube

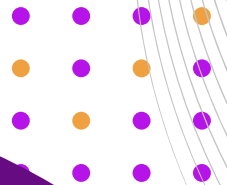

Chapter one: Introduction To machinary

all electric machines rotate around an axis, called (shaft)

⇒ Basic of Rotational motion :-

① angular position (θ) $\rightarrow$ (deg, rad).
the angle at which the object Rotate :
or oriented .

② angular velocity (ω) $\rightarrow$ (rad/s) (speed)
Rate change of angular position wR To time

ccw $\rightarrow$ $\oplus$ $\omega = \frac{d\theta}{dt}$

For electrical machines.

ω_m : angular velocity (rad/s)
" " " (rev/min)
 n_m : " " (rev/sec)
 f_m : " " (rev/sec)

①

$$n_m = 60 f_m$$

$$f_m = \frac{\omega_m}{2\pi}$$

$$n_m = \frac{60}{2\pi} \omega_m$$

③ Angular acceleration (α) $\rightarrow$ (rad/s^2)

the rate change of angular velocity.


$$\alpha = \frac{d\omega}{dt}$$

②

④ Torque (τ) $\rightarrow$ (N.m)

"Twisting force" the product of the force applied to the object and the smallest distance between the line of action of the force and the object's axis of rotation.
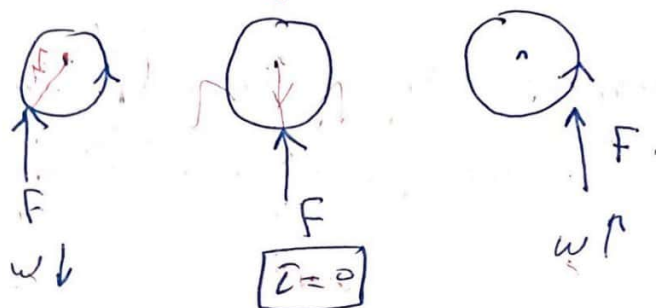
$$\tau = Fr \sin \theta \rightarrow \text{newton-meter.} \\ (\text{N.m})$$



⑤ work (w) $\rightarrow$ (J)

$$w = \int \tau d\theta \rightarrow \boxed{w = \tau \theta} \text{ Joule.}$$

⑥ power (P) $\rightarrow$ (J/s = watt)

$$P = \frac{dw}{dt} = \tau \frac{d\theta}{dt} = \tau \omega$$

rate change of work per unit time.


③

(1.4) magnetic field :-



magnetic field is used in machines (like motors and generators) and in transformers

Four Basic principles of describes how magnetic field used in these devices:-

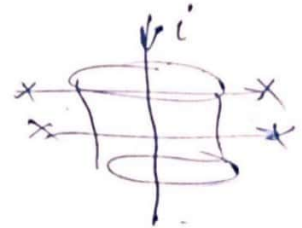- ① current-carrying wire produces a magnetic field in the area around it.



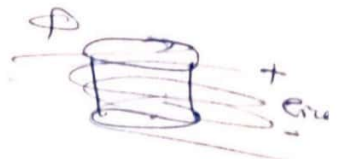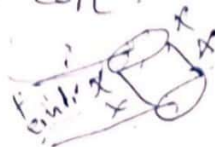
- ② time changing magnetic field induces a voltage in a coil of wire if it passes through that coil.




- ①, ② are the principles of Transformer.

(u)

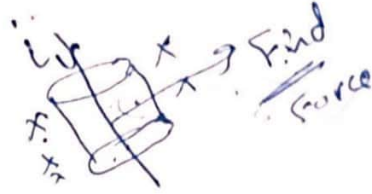- (3) A ~~an~~ current carrying wire in the presence of a magnetic field has a force induced on it (Basic of motor)



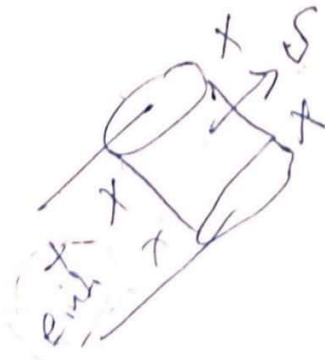- (4) A moving wire in the presence of a magnetic field has a voltage induced in it $\Rightarrow$ (Basic of Generator).



(5)

* Production of a magnetic field

Ampere's law $\int H \cdot dL = I_{\text{net}}$


H : magnetic field intensity

L : path length of the core.

I : Current.

$$H = \frac{NI}{L}$$

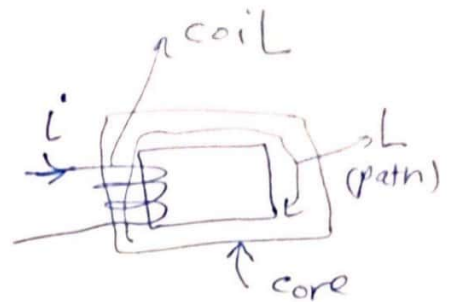current
coil of wire cuts the path
 N times.



$H \rightarrow$ Amper.Turns/m
(A.Turns/m)

the flux density in the core (B)

$$B = \mu H$$

B : flux density

μ : magnetic permeability
(henry/m)

$B \rightarrow$ henry.A.Turns/m²

$\rightarrow$ weber/m² $\Rightarrow$ Tesla (T)

μ_0 for free space $\rightarrow \mu_0 = 4\pi \times 10^{-7}$.

relative permeability $\mu_r = \frac{\mu}{\mu_0} \rightarrow$ for ferromagnetic material

* for steel $\mu_r = 2000 \rightarrow 6000$

(6)

$$B = \mu H = \frac{\mu N i}{L}$$

Total flux in the core Φ

$$\boxed{\Phi = BA} \quad \Phi = \frac{\mu N i A}{L}$$

$\Phi \rightarrow \text{weber}$

To find the total flux

in the core $\Rightarrow \frac{L_c}{\mu_i A} > \underline{\underline{\mu_{\text{known}}}}$


For ~~to simply~~

convert magnetic circuit

To Electrical circuit

for accurate calculation
of the Φ

(7)

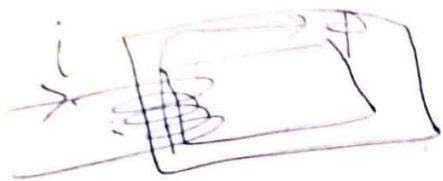


Ni is the force
to get the flux

$$F = Ni \quad \text{magnetomotive force (Ampere-Turns)}$$



$\Phi \rightarrow$ like electrical current.

path $\rightarrow$ like R
core

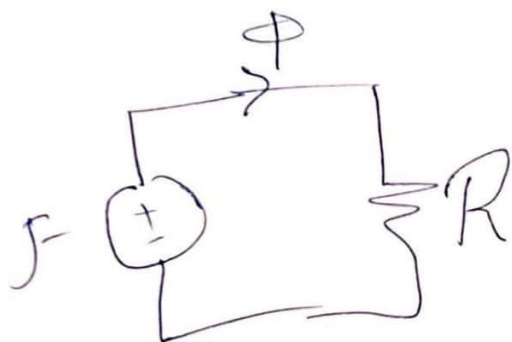

$$\Phi = BA = \frac{\mu A Ni}{L} = \left(\frac{\mu A}{L} \right) F$$

$$\Rightarrow F = \frac{\Phi R}{\mu A}$$

$$\Rightarrow R = \frac{L}{\mu A}$$

Reluctance
equivalent
to electrical
Resistance
 R

$F \rightarrow$ equivalent to V

$\Phi \rightarrow$ equivalent to I .

(8)

$$R = \frac{L}{\mu A} \quad R = \frac{F}{\Phi} = \frac{\text{Ampere} \cdot \text{turns}}{\text{weber}}$$


$$R \longrightarrow \text{Amp. Turns / wb} \text{ unit}$$


$$\rho = \frac{1}{R} \longrightarrow \text{permeance.}$$

$\Rightarrow$ R like Electrical Resistance.

for series $R_{eq} = R_1 + R_2 + \dots$

for parallel $\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots$

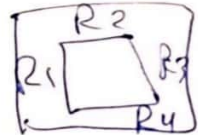Series $\leftarrow$  the same flux

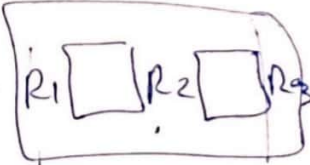
Parallel $\leftarrow$  different flux

(9)

Calculations of the flux in the core are always approximation $\rightarrow$ Reasons

- ① R is not accurate $\rightarrow$ corners
- ② μ is not constant Φ .
- ③ leakage fluxes neglected.
- ④ effect of the air gap in the core increasing area of flux.

$\Rightarrow$ fringing the air gap.

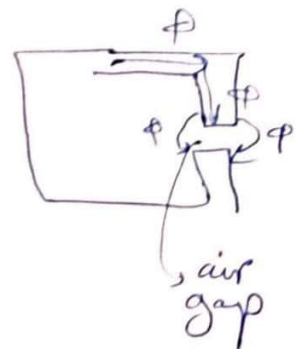

⑩

Ex

depth = 10 cm

$\mu_r = 2500$

$I = 1 \text{ A}$

find Total flux ??

$\mu = \mu_0 \mu_r$

$R_1 = \frac{L_1}{\mu A_1} \rightarrow \mu = \mu_0 \mu_r$

$L_1 = 5 + 30 + 7.5 + 7.5 + 30 + 7.5 + 7.5 + 30 + 5 = 1.3 \text{ m}$

$R_1 = \frac{1.3 \text{ m}}{(4\pi \times 10^{-7})(2500)(0.015)}$

$R_1 = 27600 \text{ A.turns/wb}$

قوسين كوسين
Cm $\rightarrow$ m

$L_1 \rightarrow A_1 = 15 \times 10$

$L_2 \rightarrow A_2 = 10 \times 10$

Area = depth $\times$ y

center to center no L_1 $\leftarrow$

$R_2 = \frac{L_2}{\mu A_2}$


$= \frac{7.5 + 30 + 7.5}{(4\pi \times 10^{-7})(2500)(0.01)} = \frac{0.45}{(4\pi \times 10^{-7})(2500)(0.01)} = 14300 \text{ A.turns/wb}$

R_1, R_2 series



$R_{eq} = R_1 + R_2$

$\Phi = \frac{F}{R_{eq}} = \frac{NI}{R_{eq}} = 0.0048 \text{ wb}$

(11)

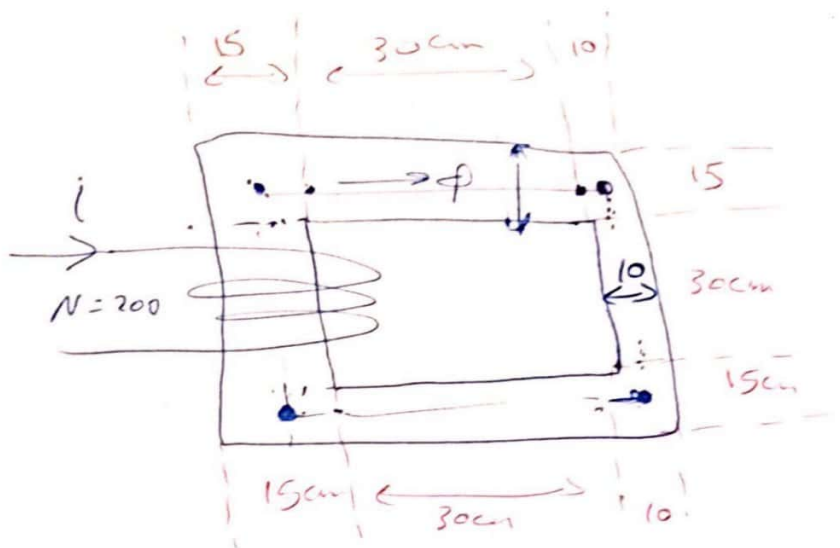

Area $\rightarrow$ depth $\times$ y

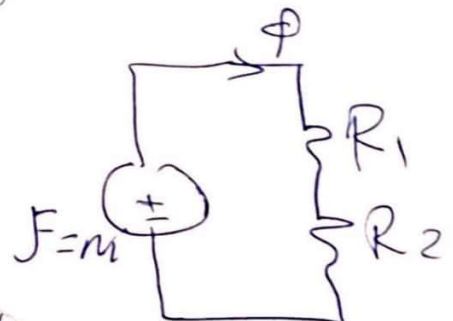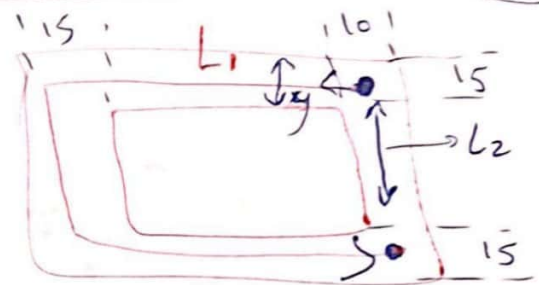

(ex)

$$L_c = 40 \text{ cm}$$

$$\text{Area} = 12 \text{ cm}^2 = A_c$$

$$\mu_r = 4000$$

if fringing in the air

gap Increasing Area by 5%.

And i to get 0.5 T in the air gap??

$$R_{\text{core}} = \frac{L_c}{\mu A_c} = \frac{(40 \times 10^{-2})}{(4000)(4\pi \times 10^{-7})(12 \times 10^{-4})}$$

$$R_{\text{core}} = 66300 \text{ A.turns/Wb}$$



$$R_g = \frac{L_g}{\mu_0 \mu_r A_g} = \frac{(0.05 \times 10^{-2})}{(4\pi \times 10^{-7})(A_g)}$$

$$R_g = \frac{(0.05 \times 10^{-2})}{(4\pi \times 10^{-7})(12.6 \times 10^{-4})} = 316000 \text{ A.turns/Wb}$$

$$R_{\text{eq}} = R_g + R_{\text{core}}$$

$$B = 0.5 \text{ T}$$

$$\Rightarrow i = 0.602 \text{ A}$$

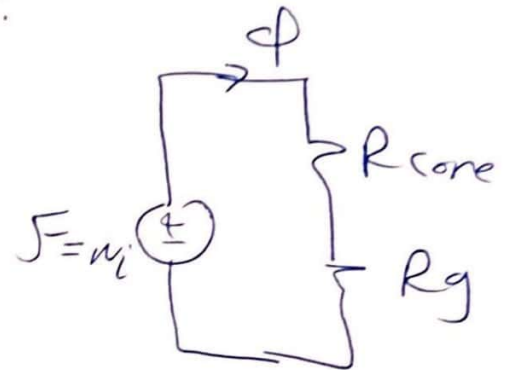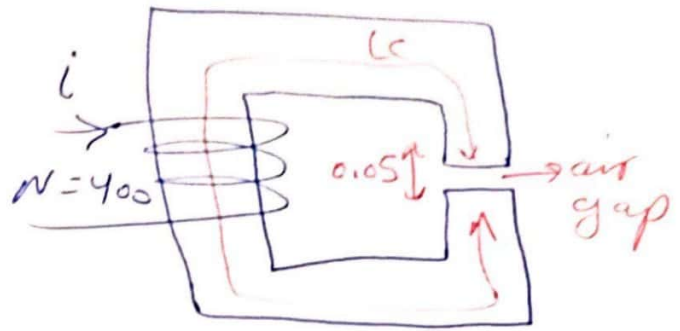

$A_g = \text{Area of the air gap}$

$$A_g = A_c + 5\% A_c = 12 + \frac{5}{100} \times 12$$

$$A_g = 12.6 \text{ cm}^2$$

$$\Phi = BA = \frac{F}{R_{\text{eq}}} = \frac{Ni}{R_{\text{eq}}}$$

(12)

* Behavior of ferromagnetic material.


If a DC current is applied to the core.

$$\text{if } i \uparrow \rightarrow F = NI \uparrow \rightarrow \Phi \uparrow$$

small increase in $I \rightarrow$ huge increase of Φ

then if $I \uparrow \rightarrow F \uparrow \rightarrow \Phi \uparrow$ but with small amount.

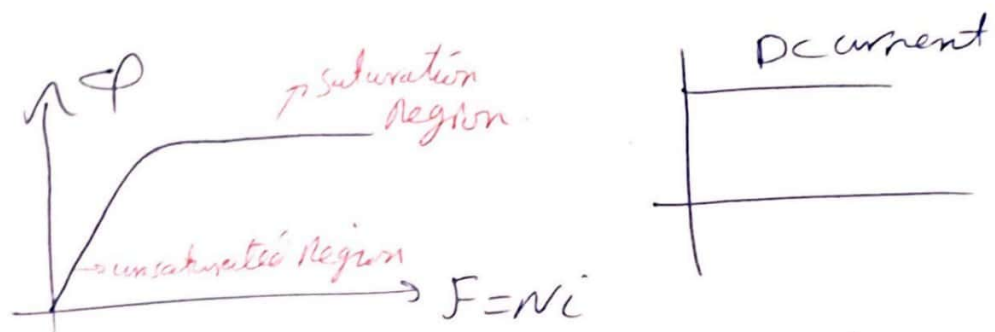until reach a certain $I \rightarrow$ then Φ still constant.



saturation curve or magnetization curve


$$H = \frac{NI}{L} \rightarrow \frac{F}{L} \rightarrow$$

$$\Phi = BA \rightarrow \mu B = \frac{\Phi}{A}$$


$$\text{Slope} = \frac{B}{H} = \mu$$

Note that μ is not constant with I .

through core.

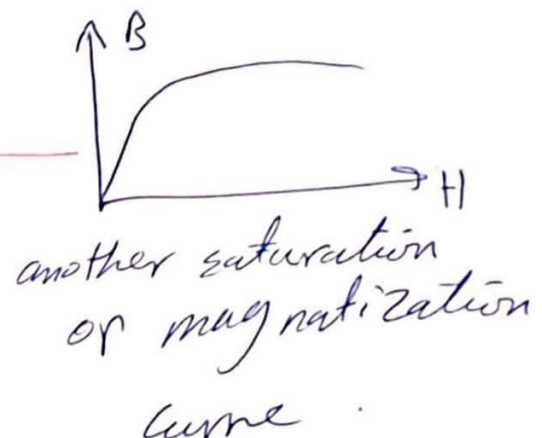

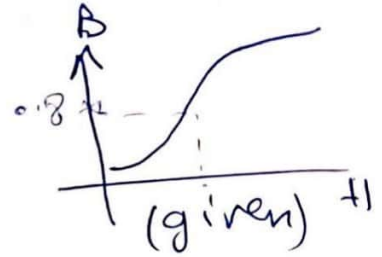ex Square magnetic core has $L = 55 \text{ cm}$
and $A = 150 \text{ cm}^2$, 200 turns
 N



- ① How much current is required to produce 0.12 Wb ?

$$B = \frac{\Phi}{A} = 0.8 \text{ T} \rightarrow \text{from fig at } B = 0.8 \text{ T} \\ H = 115 \text{ from curve.}$$

$$F = NI = HL \rightarrow H = \frac{NI}{L}$$

$$\Rightarrow I = 0.316 \text{ A}$$

- ② The μ .

$$\mu = \frac{B}{H} = 0.00696 \text{ H/m.}$$

$$\mu_r = \frac{\mu}{\mu_0} = 5540.$$

- ③ Reluctance

$$R = \frac{F}{\Phi} = 5270 \text{ A.T/Wb} = \frac{NI}{\Phi}$$


(14)

* Energy losses in a ferromagnetic core.


If an AC current is applied to the core st

Assume $\Phi = 0$.

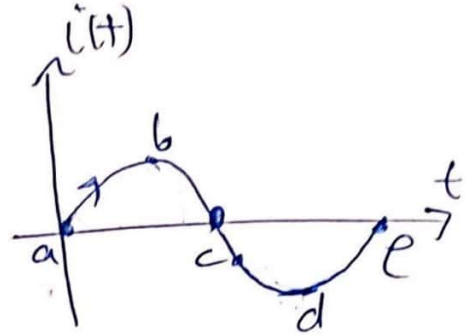① If i increased from $a \rightarrow b$
Flux in the core will
increased from $a \rightarrow b$.



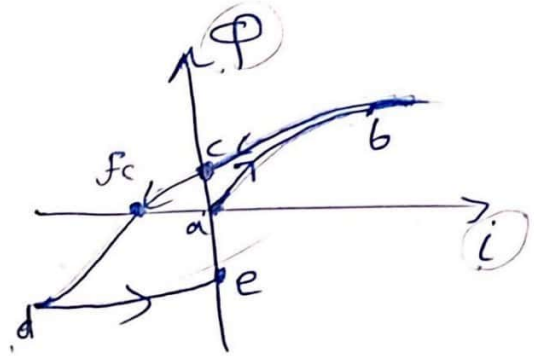② after ① the current falls
again $\rightarrow$ the flux also falls
but with different path



③ If $I = 0$ at Point ③

the flux in the core is not

$$\text{Zero} \Rightarrow i = 0 \Rightarrow \Phi \neq 0$$

point ③ $\Rightarrow$ this value


called Residual flux Φ_{res}

④ If current increases but with negative
value $\Rightarrow \Phi$ increase in opposite direction
(15)

if I at point (a)
 Φ at point (d)

note that the flux takes different paths.

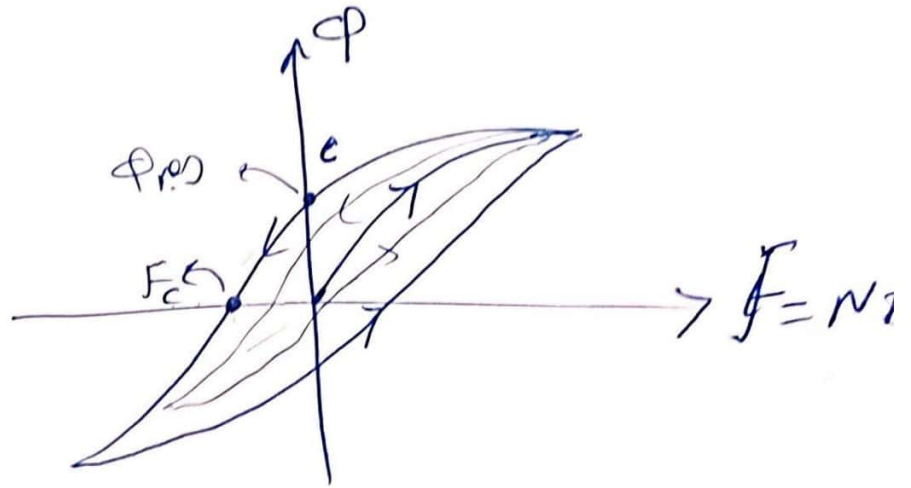Relation between
 $\Phi, I \Rightarrow$
 called
 hysteresis loop.



hysteresis loop


always the flux takes different path.
 for the same value of the current.

- point c $\rightarrow \Phi_{res}$: Residual flux
 Residual. $\Phi = \Phi_{res} \Rightarrow i = 0$
 $F = 0$
- F_c : coercive force : the force need to
 force the flux to zero, applied to
 the core in the opposite direction.

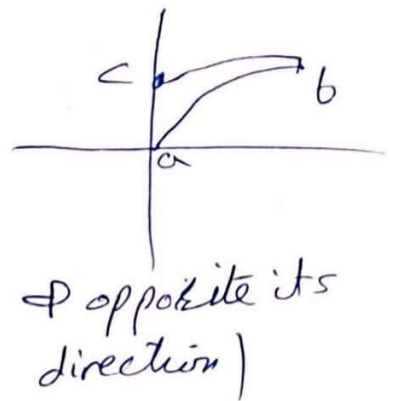
(16)

* Why hysteresis *

- ① within Ferromagnetic materials There's are many small regions called domains, each domain acts as a small permanent magnet, oriented randomly within the material. So total flux = 0
- ② if an external field is applied to ferromagnetic material, some of the domains will oriented toward the external field (Randomly)
- ③ if $i \uparrow \Rightarrow \Phi \uparrow$ more domains oriented toward the field (external) until ~~Rea~~ all domains oriented toward the external field $\Rightarrow$ reach saturation (a $\rightarrow$ b)
- ④ if the $i \downarrow \rightarrow$ some of domains reoriented toward the flux in opposite direction (as $i \downarrow \Rightarrow \Phi$ opposite its direction)
- ⑤ if $i = 0 \Rightarrow \Phi = 0$ some domains still oriented toward the flux (point c)
 $\Rightarrow \Phi_{res}$.



(17)

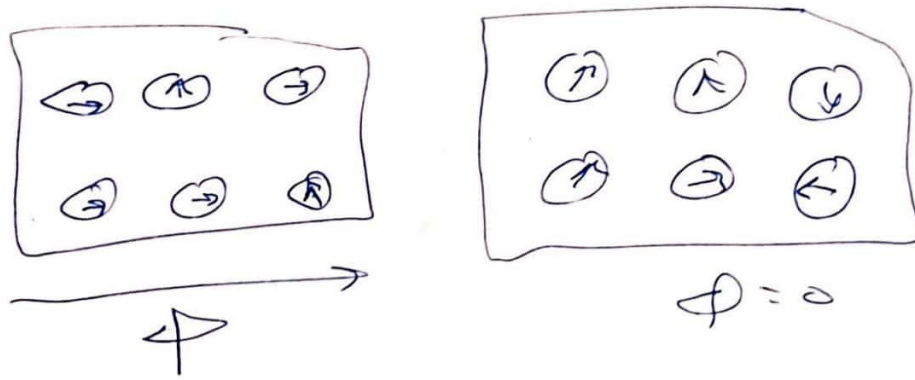


- we need coercive force F_{cor} to reorient all domains $\Rightarrow$ loss

- hysteresis loss: energy required to accomplish the reorientation of domains during each cycle of the AC current applied to the core.

(1.5) Induced voltage from time changing flux.

$$e_{ind} = - \frac{d\phi}{dt}$$

$$e_{ind} = -N \frac{d\phi}{dt}$$

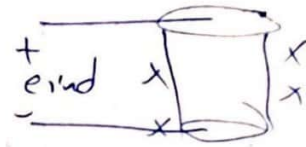

time changing flux induces voltage within the core as that within the coil

These voltages cause swirls of current within the core

like eddies $\rightarrow$ eddy currents.

$\Rightarrow$ eddy current flow within the resistive core. $\rightarrow$ so energy dissipated

$\Rightarrow$ heat.

To decrease the effect of eddy currents:

① Core is broken into strips or laminations to get small Area for the current.

② Add Insulating material between strips (or)


③ Core loss $\left\{ \begin{array}{l} \text{eddy current loss} \\ \text{hysteresis loss} \end{array} \right.$

(19)

(1.6) current-carrying wire in presence of Φ
 produce a force in the wire.

$$F_{ind} = i L \times B$$

$$F_{ind} = i L B \sin \theta$$

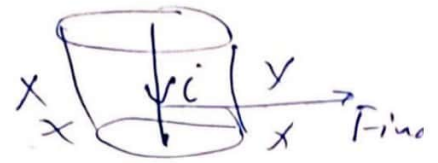


$\Rightarrow$ Motor Action

(1.7) moving wire in presence of $\Phi \Rightarrow$ end



$$e_{ind} = v \times B \cdot L$$

$$= v B \sin \theta L \cos \phi$$

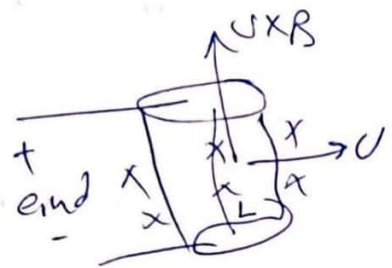

$\Rightarrow$ Generator Action

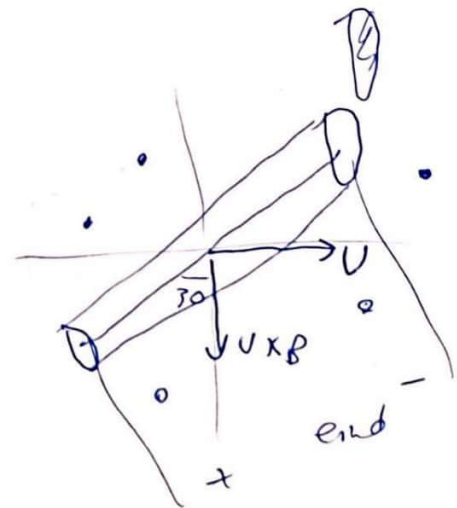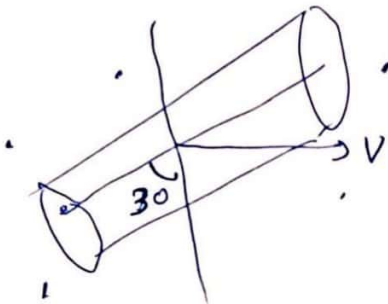ex $e_{ind} = v B \sin 90^\circ L \cos 30^\circ$



(20)

2.7) Voltage Regulation and efficiency.

(1)

V_o changes with load even if V_{in} is constant.


Full load voltage regulation: is a quantity that compares the output voltage of the transformer at no load with the output voltage at full load.

$$V_R = \frac{V_{sNL} - V_{sFL}}{V_{sFL}} \times 100\%$$

at no load $V_{sNL} = V_P/a$

For Ideal transformer $V_{sNL} = V_{sFL}$

$$V_R = 0$$

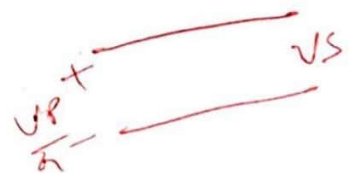

For Real transformer


$$V_{sNL} \neq V_{sFL}$$

$$V_R < 0$$

$$V_R > 0$$

(2)

eq circuit Referred To secondary side

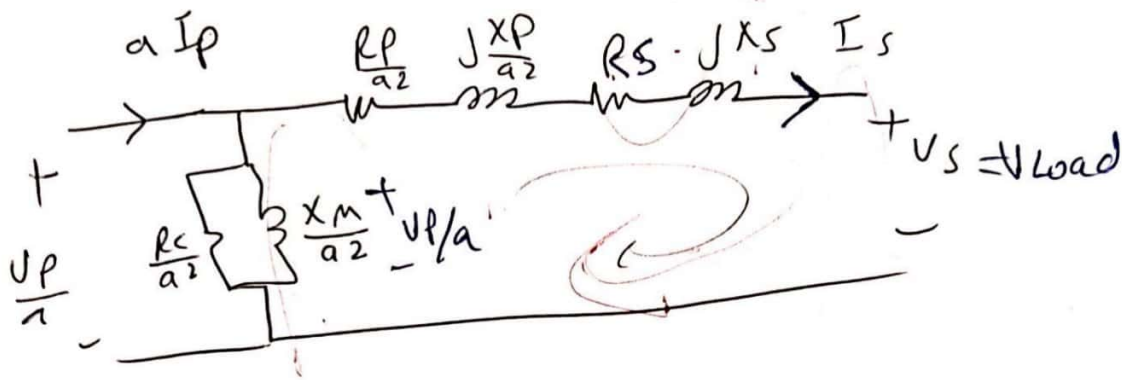

by KVL

$$V_{s_{NL}} = \frac{V_p}{a} = I_s (R_{eqs} + jX_{eqs}) + V_s$$

$$R_{eqs} = \frac{R_p}{a^2} + R_s$$

$$X_{eqs} = X_s + j\frac{X_p}{a^2}$$

$$V_s = V_s \cos \phi$$

$$\frac{V_p}{a} = V_{sNL}$$

V_{sNL} change with power factor.

① for lagging power factor $I_s = I_s \angle -\theta$

$$V_{sNL} = \frac{V_p}{a} > V_s \cos \phi$$

$$V_R > 0$$

(22)

② for leading power factor

$$I_s = I_s / +\theta$$

$$V_{snL} < V_s fL$$

$$\boxed{V_R < 0}$$

③ for unity pf. $I_s = I_s / 0$

$$V_{snL} \overset{is}{\cancel{<}} V_s fL$$

$$\boxed{V_R > 0}$$

$$\text{efficiency: } \eta = \frac{P_o}{P_{in}} \times 100\%$$

$$P_o = V_s I_s \text{ pf}$$

$$P_{in} = P_o + P_{loss}$$

$$P_{loss} = P_{cu} + P_{core}$$

$$P_{cu} = |I_s|^2 R_{eqs}$$

$$P_{core} = \frac{(V_{p/a})^2}{R_{cs}}$$

$$R_{cs} = \frac{R_c}{a^2}$$

③

Ex 15 kVA, 2300/230V, Power Transformer.
Power VP VS

open circuit test (at LVs) $V_{oc} = 230V$ $I_{oc} = 2.1A$ $P_{oc} = 50W$

short circuit test (HV) $V_{sc} = 47V$ $I_{sc} = 6A$ $P_{sc} = 160W$

- ① find equivalent circuit Referred to LVs.
- ② calculate VR at 0.8 lag, lead pf and unity pf
- ③ η at 0.8 lagging pf.

From open circuit test

$$Y_{oc} = \frac{I_{oc}}{V_{oc}} \angle -\theta$$

∠ = $\cos^{-1} \frac{P_{oc}}{V_{oc} I_{oc}} = 84^\circ$

$$Y_{oc} = 0.00913 \angle -84$$

this test at LVs $\rightarrow$ secondary

$$R_{cs} = 0.00913 \cos -84 = 1050 \Omega$$

$$X_{ms} = 0.00913 \sin -84 = 110 \Omega$$

$$R_c = a^2 R_{cs} = 105 k$$

$$X_m = a^2 X_{ms} = 11 k\Omega$$

$$a = \frac{V_P}{V_S} = \frac{2300}{230}$$

$$Z_P = a^2 Z_S$$

2/11)

From short circuit test

$$Z_{sc} = \frac{V_{sc}}{I_{sc}} \angle \theta$$

$$\theta = \cos^{-1} \frac{P_{ss}}{V_{sc} I_{sc}}$$

$$Z_{sc} = 7.833 \angle 55.4^\circ$$

$$= \underbrace{4.45}_{R_{eqp}} + j \underbrace{6.45}_{X_{eqp}}$$

← this test at
(HVS)
Primary

$$R_{eqp} = 4.45 \rightarrow R_{eqs} = \frac{R_{eqp}}{a^2} = 0.0645 \Omega$$

$$X_{eq} = 6.45 \rightarrow \frac{X_{eqs}}{a^2} = \frac{X_{eqp}}{a^2} = 0.0645 \Omega$$



To find V_R and η

$$V_{sPL} = V_s = 230V \leftarrow \text{تولید توان}$$

$$I_s = \frac{S}{V_s} = \frac{15k}{230} = 65.2 A$$

① at 0.8 lag

$$I_s = 65.2 \angle -\cos^{-1} 0.8$$

$$= 65.2 \angle -36.87^\circ A$$

(25)

$$V_{sNL} = \frac{V_P}{a} = I_S(R_{eqs} + jX_{eqs}) + V_{sfl}$$

$$= 65.2 \angle -36.87^\circ (0.0445 + j0.0645) + 230$$

$$V_{sNL} = \frac{V_P}{a} = 234.85 \angle 0.4^\circ > \underbrace{230}_{\text{lagging}} = V_{sfl}$$

$$V_R = \frac{V_P/a - V_{sfl}}{V_{sfl}} \times 100$$

$$V_R = \frac{234.85 - 230}{230} \times 100\% = \underline{2.1\%} > 0$$

② at 0.8 leading P f $V_{sfl} = 230V$ ≈ 230

$$I_S = 65.2 \angle +\cos^{-1} 0.8$$

$$I_S = 65.2 \angle 36.87^\circ$$

$$\frac{V_P}{a} = V_{sNL} = I_S(R_{eqs} + jX_{eqs}) + \underbrace{V_{sfl}}_{230}$$

$$\frac{V_P}{a} = 229.85 \angle 1.24^\circ < \underline{230} \text{ leading}$$

$$\boxed{V_R = -0.06\%} < 0$$

③ at P f = 1

$$\boxed{V_{sfl} = 230V}$$

$$I_S = 65.2 \angle 0$$

نوعه بنفشه الکترولیت $V_{sAL} = \frac{V_P}{a} = 232.9 \angle 1.04^\circ > \underbrace{V_{sfl}}_{230}$

$$\boxed{V_R = 1.28\%} > 0$$

(66)

③ η at 0.8 lagging
 $I_s = 65.2 \angle -36.87^\circ$

$V_s = 230$

$\frac{VP}{a} = 234.85$

$P_o = V_s I_s \cos \phi$
 $= (230)(65.2)(0.8)$

$P_o = 12 \text{ kW}$

$P_{cu} = |I_s|^2 R_{eqs} = (65.2)^2 (0.0445) = 189 \text{ W}$ *per VS*

$P_{core} = \frac{(VP/a)^2}{R_{cs}} = \frac{(234.85)^2}{1050} = 52.5 \text{ W}$

$P_{in} = P_o + P_{cu} + P_{core}$

$\eta = \frac{P_o}{P_{in}} \times 100\% = 98.03\%$

Note that

$P_{cu} = 189 \approx$

$P_{sc} = 160 \text{ W}$
 test no
 short circuit
 test *copy for k*

$P_{core} = 52.5 \text{ W} \approx$

$P_{oc} = 50 \text{ W}$

from
 open circuit
 test
 core loss



27

Chapter Two: Real and Ideal transformer.

* Transformer is a device that changes ac electric power at one voltage level to another voltage level, through the action of magnetic field.

* It consists of two or more coils of wire wrapped around a ferromagnetic material core.

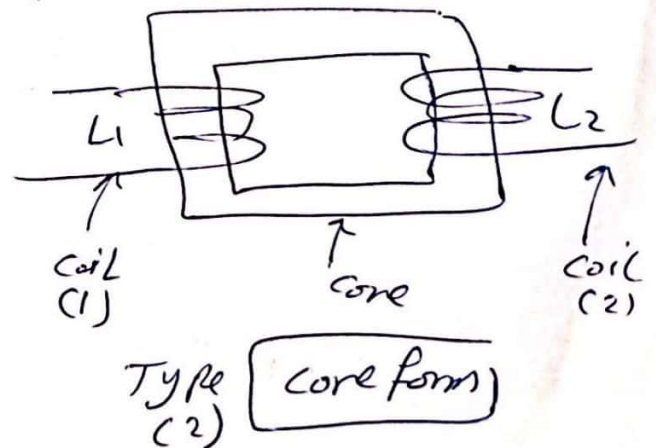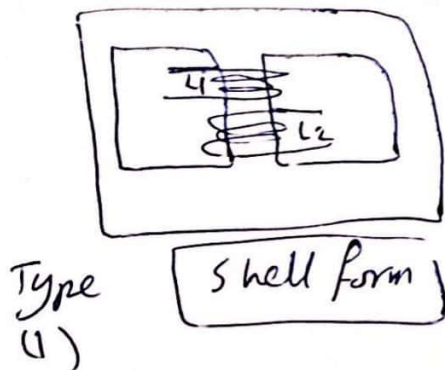
⇒ no electrical connection between coils.




①

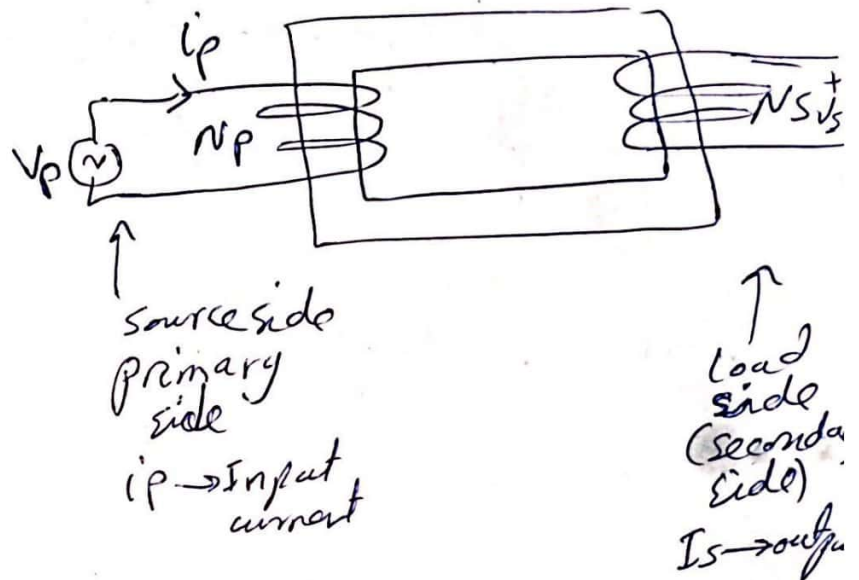2.3 the Ideal transformer:-

is a lossless device with an Input winding and an output winding (L_1, L_2).



schematic symbol of Transformer

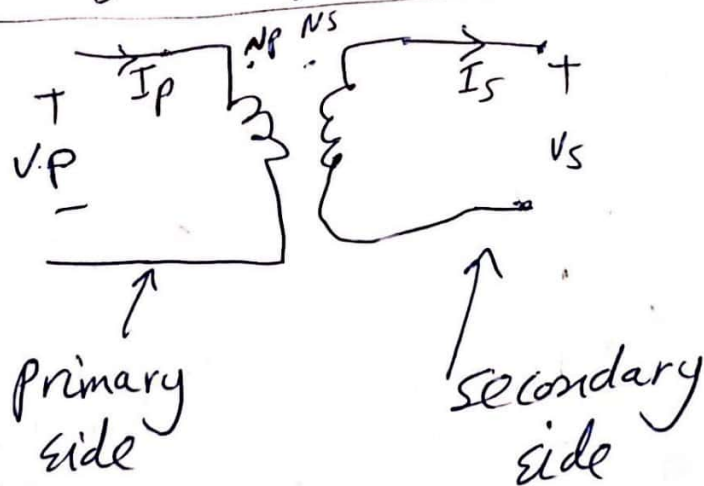


(2)

For an ideal transformer.

⇒ find Relations between V_P, V_S and I_P, I_S , Z_P, Z_S and power
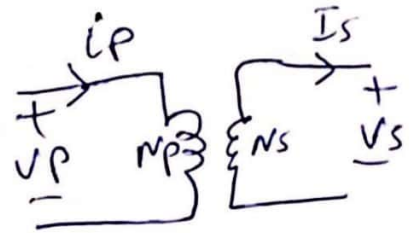
$$\frac{V_P(+)}{V_S(+)} = \frac{N_P}{N_S} = a$$



$$a = \frac{N_P}{N_S} \rightarrow \text{turns ratio}$$

$$\boxed{V_P = a V_S}$$

If $a > 1 \Rightarrow V_P > V_S$ step down

If $a < 1 \Rightarrow V_P < V_S$ step up.

If $a = 1 \Rightarrow V_P = V_S \rightarrow \text{unity}.$

$$N_P I_P = N_S I_S$$

$$\frac{I_P}{I_S} = \frac{N_S}{N_P} = \frac{1}{a}$$

$$\boxed{I_P = \frac{I_S}{a}}$$

(5)

Input Impedance Z_p

$$Z_p = V_p / I_p$$

$$Z_s = V_s / I_s$$


Z_{pZ} $V_p = a V_s$ $I_p = \frac{I_s}{a}$ $\nearrow$ i.e.

$$Z_p = (a V_s) / \left(\frac{I_s}{a} \right)$$

$$Z_p = a^2 \frac{V_s}{I_s} = a^2 Z_s$$

$$\boxed{Z_p = a^2 Z_s}$$

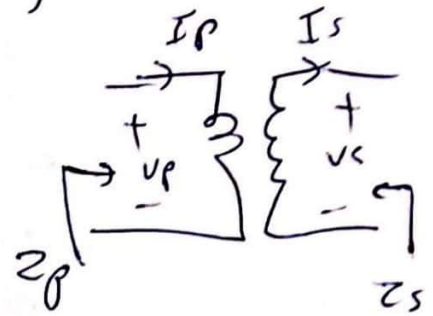reflected Impedance
from secondary
To primary side



$\Rightarrow$ for the power

$$P_{in} = V_p I_p \cos \theta \longrightarrow \text{Average or Real power}$$

$$P_o = V_s I_s \cos \theta$$

$$\begin{aligned} V_p &= a V_s \text{ (i.e.)} \\ I_p &= \frac{I_s}{a} \end{aligned}$$

$$\boxed{PF = \cos \theta}$$

$$\boxed{P_{in} = P_o} \text{ for Ideal Transformer}$$

(4)

for Reactive power Q .

$$Q_{in} = V_p I_p \sin \theta \quad \leftarrow \begin{cases} V_p = a V_s \\ I_p = \frac{I_s}{a} \end{cases}$$

$$Q_o = V_s I_s \sin \theta$$

$$\boxed{Q_{in} = Q_o} \quad \text{Ideal Trans.}$$

for Apparent power S .


$$S_{in} = V_p I_p \quad S_o = V_s I_s$$

$$\boxed{S_{in} = S_o} \quad \text{Ideal Transf.}$$

To Analyze any electrical circuit contains
transformer $\Rightarrow$ take an equivalent
for the Transformer.

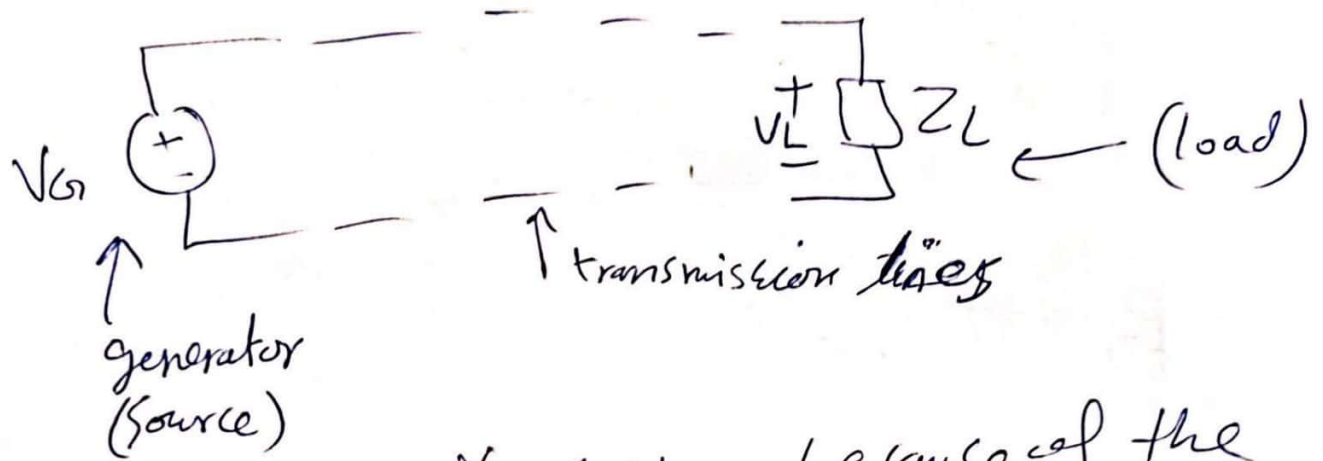(5)

Transformer used to reduce losses
through transmission lines



$V_L < V_G$ because of the
losses in the lines

To solve this problem $\rightarrow$ transformer
used to increase $V_G \Rightarrow$ so losses
decreased through lines

as shown in example below

6

ex

A single power system as shown.

① find V_{Load} .

$$I_G = \frac{V_G}{Z_{eq}}$$


$$= \frac{480 \angle 0^\circ}{0.18 + j0.24 + 4 + j3}$$

$$I_G = 90.8 \angle -37.8^\circ \text{ A}$$

$$V_{Load} = I_G Z_{Load}$$

$$= (90.8 \angle -37.8^\circ)(4 + j3)$$
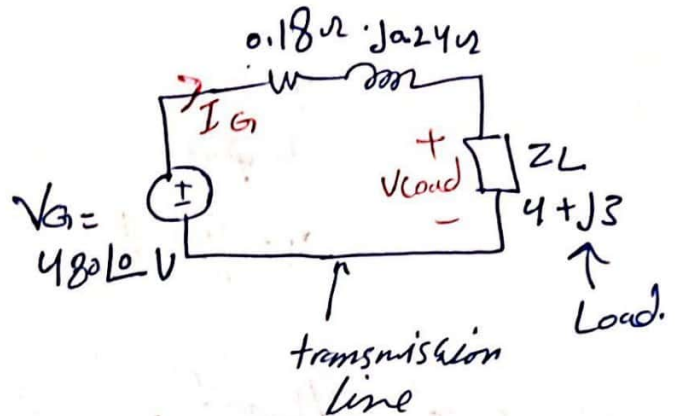
$$V_{Load} = 454 \angle -0.9^\circ \text{ V}$$



$$4 + j3 \rightarrow 5 \angle 36.9^\circ$$


② find transmission line losses = power loss.

$$\Rightarrow P_{loss} = |I_G|^2 (R_{line})$$

$$P_{loss} = (90.8)^2 (0.18) = 1484 \text{ W}$$

P_{loss} is high and V_L is low
to decrease losses $\rightarrow$ use
transformer after V_G (step
up) and step down Tr after
before (load)

(7)

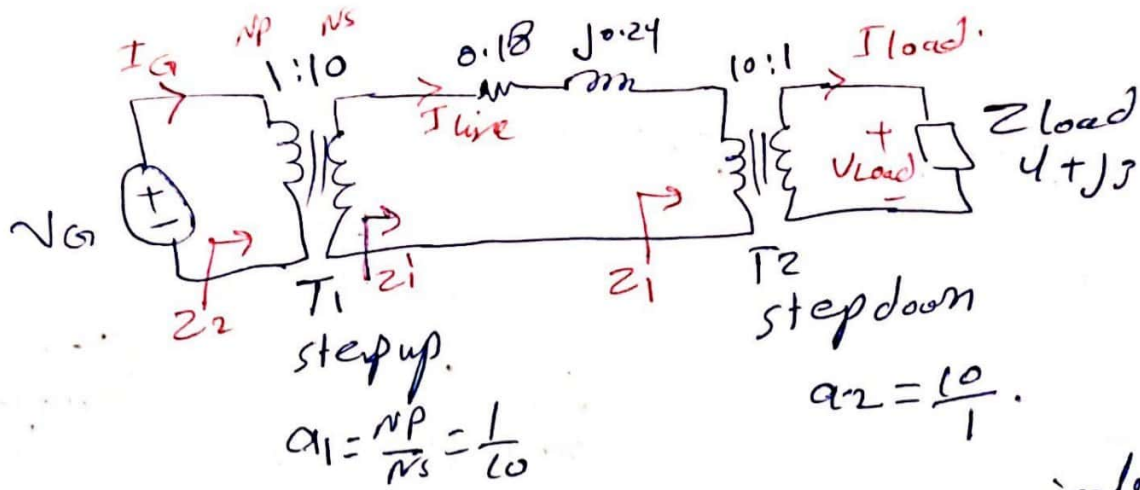

① find V_{Load} → we must find equivalent Impedance ($Z_p = a_2^2 Z_s$)

$$Z_1 = a_2^2 Z_{load}$$

$$Z_1 = 400 + j300$$



$$Z_1' = 0.18 + j0.24 + 400 + j300$$

$$Z_1' = 400.18 + j300.24$$

$$\text{Now } Z_2 = a_1^2 Z_1'$$

$$Z_2 = \left(\frac{1}{10}\right)^2 (400.18 + j300.24)$$

$$Z_2 = 4.0018 + j3.0024$$

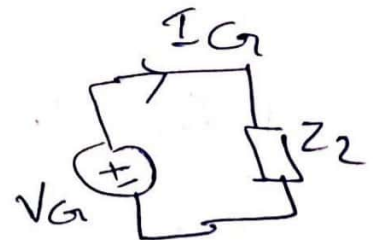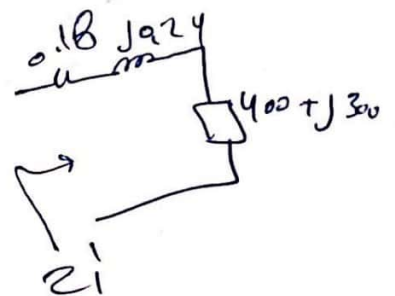

$$\text{Now } I_G = \frac{V_G}{Z_2}$$

$$I_G = \frac{480 \angle 0^\circ}{4.0018 + j3.0024}$$

$$I_G = 95.94 \angle -36.88^\circ$$

(8)

Now To find I line

$$I_p = \frac{I_s}{a}$$

$$I_{line} = \frac{I_G}{a_1} a_1$$

$$I_{line} = 9.594 \angle -36.88$$

To find I_{load} .

$$I_{load} = a_2 I_{line}$$

$$I_{load} = 95.94 \angle -36.88$$

$$V_{load} = I_{load} Z_{load}$$

$$= (95.94) \angle -36.88 (4 + j3)$$

$$V_{load} = 449.7 \angle -0.21 \text{ V}$$

② P_{loss} → losses in transmission line

$$P_{loss} = |I_{line}|^2 R_{line}$$

$$P_{loss} = (9.594)^2 (0.18) = 16.7 \text{ W}$$


* Note that loss is reduced with transformer
with Trans → $P_{loss} = 16.7 \text{ W}$
without Trans → $P_{loss} = 1484 \text{ W}$

9

② Leakage fluxes losses:-

- leakage fluxes: fluxes leave core to the air (Φ_L)


$\Phi_{LP} + \Phi_{LS}$

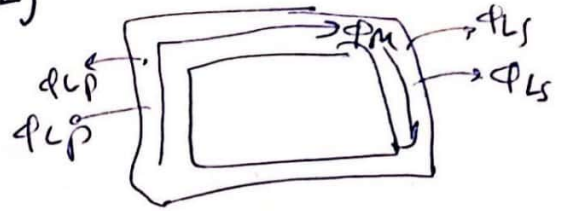

→ Φ_m : Mutual flux that links

primary and secondary coils (Φ_m)
(flux remains in the core)

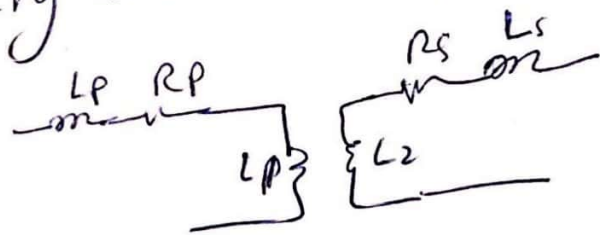these fluxes produce a self Inductance in the primary and secondary coils.
(L_P, L_S)



L_P : primary self Inductance.

L_S : ~~primary~~ secondary self Inductance.

$$Z_P = j\omega L_P = jX_P$$

$$Z_S = j\omega L_S = jX_S$$

→ Impedance.

(11)


③ eddy current losses: resistive heating losses in the core of the Transformer.

④ ~~eddy current~~

④ Hysteresis loss: rearrangement of the magnetic domains in the core.

Core loss $\begin{cases} \text{eddy loss} \\ \text{hysteresis loss} \end{cases}$

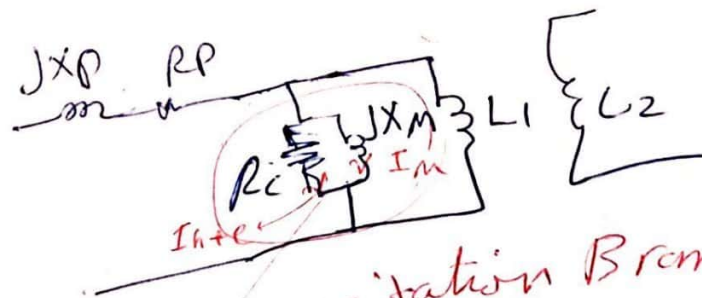Core loss can modeled by an excitation Branch which is parallel with the primary core.




excitation Branch.
 R_c → loss heat loss of the core.
 X_m : magnetization reactance.


(12)

So the equivalent Impedance of the real Transformer.


Real $\Rightarrow$ Ideal Transformer.

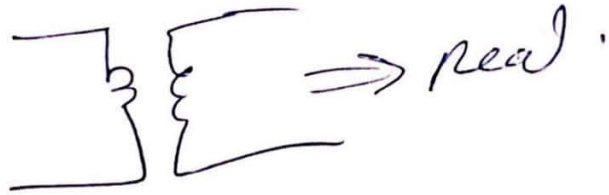


Ideal $\Rightarrow$

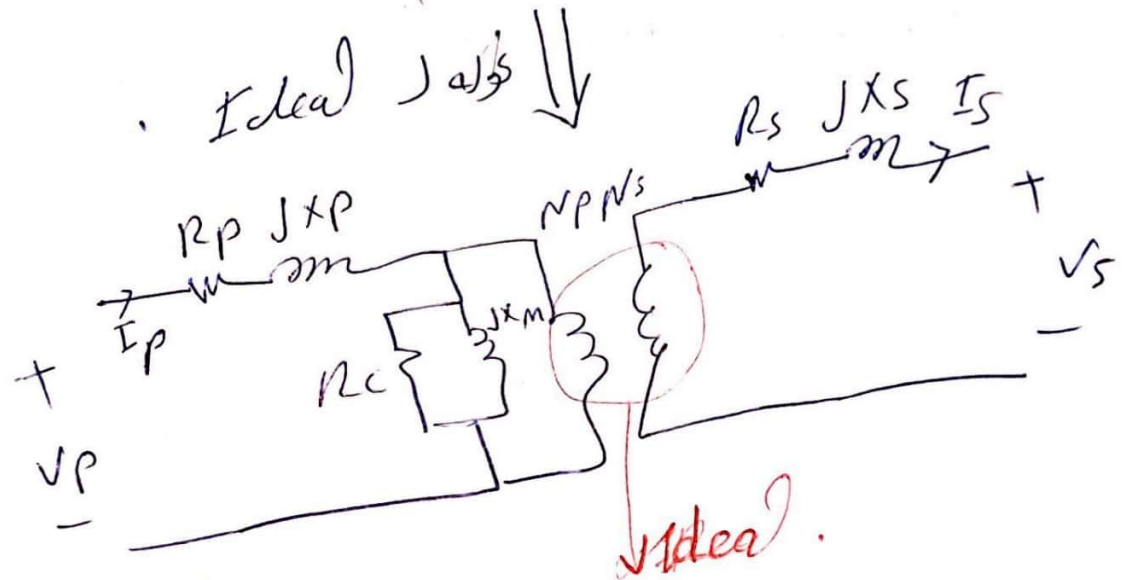

* equivalent referred to primary side :-



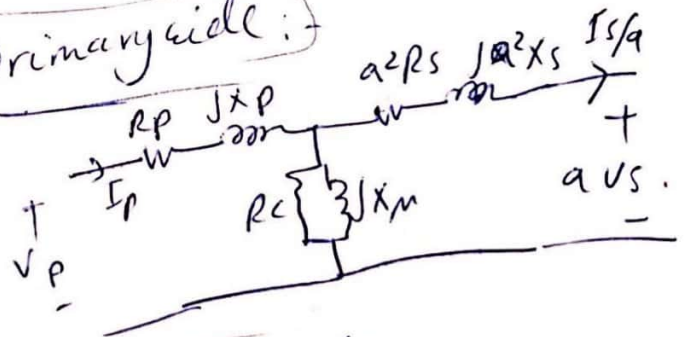


* equivalent referred to secondary side

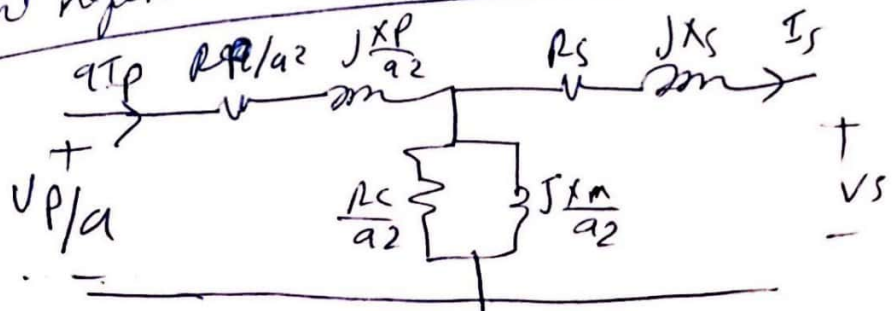

(13)

Approximate equivalent circuit

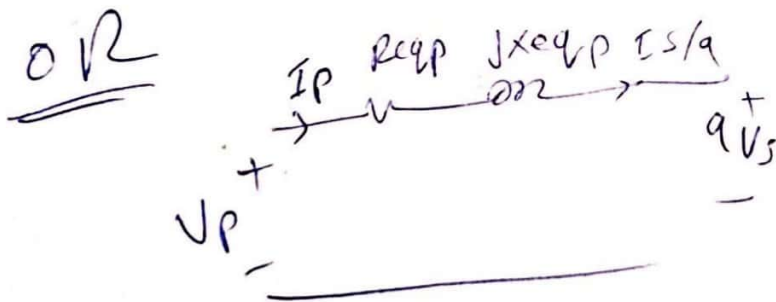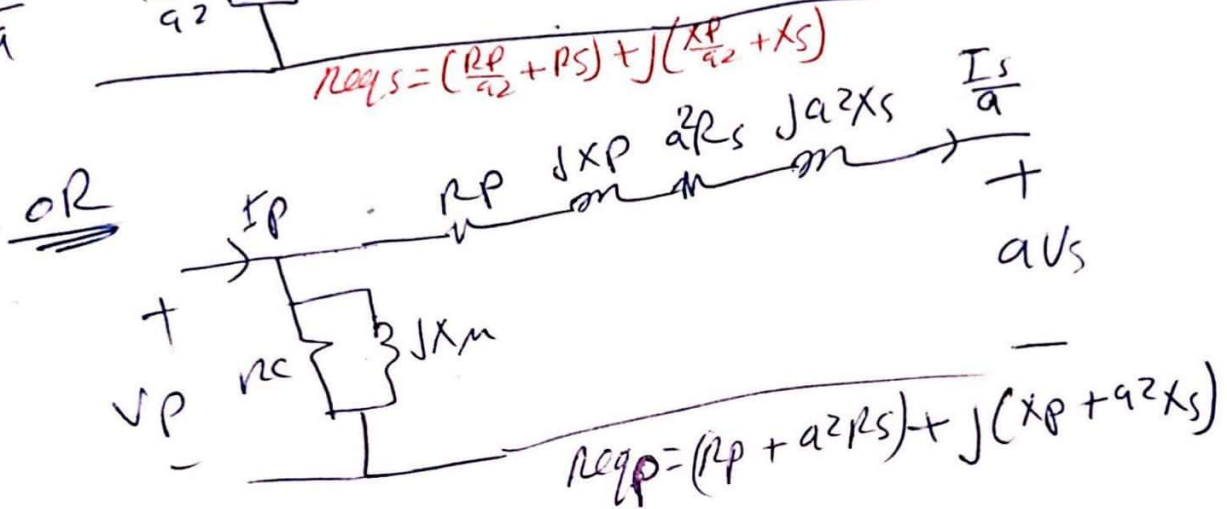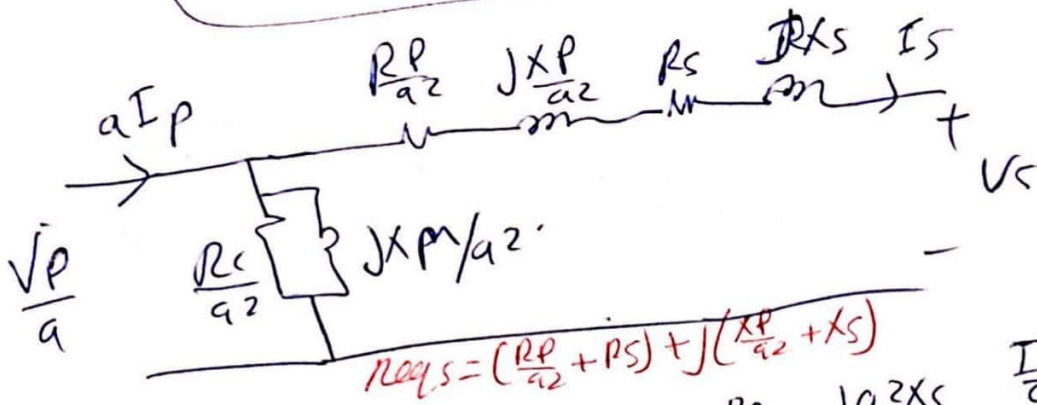

(14)

To find the components of Real Transformer we have three Tests:-

- ① open circuit test
- ② Short circuit test
- ③ DC Test

① open circuit Test

Test apply to the low Voltage side (LVS)

⇒ High voltage side still open (HVS)

* If we apply Test on primary side

find V_{oc} , I_{oc} , P_{oc} .



⇒ practical value

$$Z_{in} = R_p + jX_p + R_c \parallel jX_m$$

$$\begin{matrix} R_p \ll R_c \\ X_p \ll X_m \end{matrix}$$

so $Z_{in} \approx R_c \parallel jX_m$

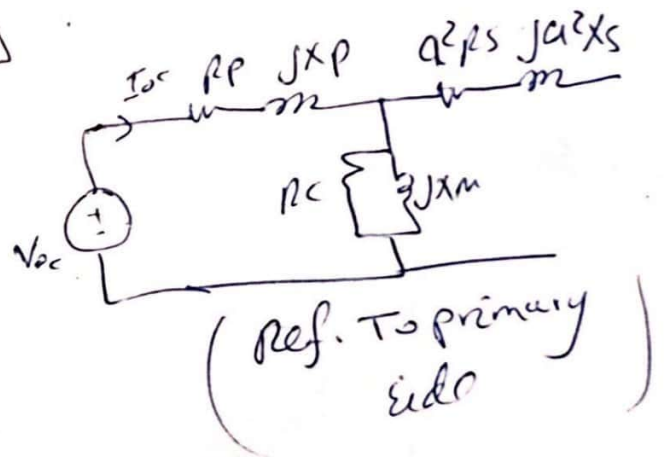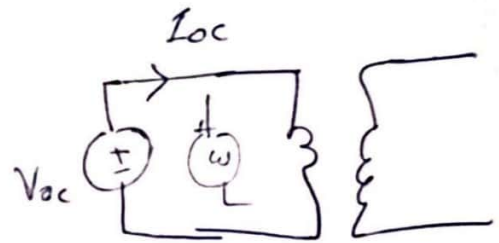use $Y_{oc} = \frac{1}{Z_{in}} = \frac{1}{R_c} - \frac{j}{X_m}$



$$V_{oc} = \frac{1}{R_c} - \frac{I}{X_m}$$

$$V = \frac{1}{Z} = \frac{I}{V}$$

$$V_{oc} = \frac{I_{oc}}{V_{oc}} \angle -\theta$$

$$P_{oc} = V_{oc} I_{oc} \cos \theta$$

$$\Rightarrow \theta = \cos^{-1} \frac{P_{oc}}{V_{oc} I_{oc}}$$

$$V_{oc} = \frac{I_{oc}}{V_{oc}} \angle -\theta = \frac{1}{R_c} - \frac{I}{X_m}$$

$$\left. \begin{aligned} \frac{1}{R_c} - \frac{I_{oc}}{V_{oc}} \cos -\theta &\rightarrow R_c \\ \frac{1}{X_m} = \frac{I_{oc}}{V_{oc}} \sin -\theta &\rightarrow X_m \end{aligned} \right\}$$

by using open circuit Test we find R_c and X_m so we can find

Loss in the core.

$$P_{oc} \approx P_{core loss}$$

(16)


② Short circuit TEST:-

Apply to the High voltage side (HVS)

→ (LVS) still a p.p.m. short.

If the test Apply to the primary


take V_{sc} , I_{sc}
 P_{sc}

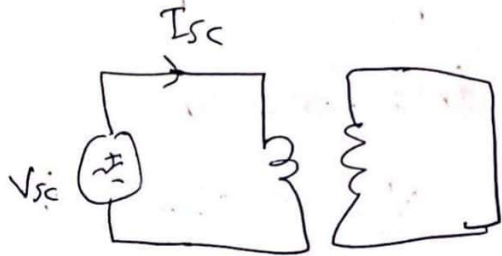

$$Z_{in} = R_p + jX_p + R_c \parallel jX_m \parallel Z_s$$

$$Z_s = a^2 R_s + ja^2 X_s$$

$$Z_s \ll R_c$$

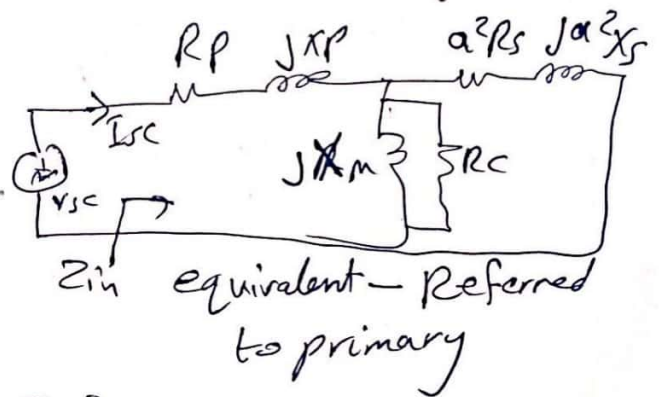

$$\Rightarrow Z_{in} = R_p + jX_p + a^2 R_s + ja^2 X_s$$

$$Z_{in} = \underbrace{(R_p + a^2 R_s)}_{R_{eqp}} + j \underbrace{(X_p + a^2 X_s)}_{X_{eqp}}$$

$$Z_{in} = R_{eqp} + jX_{eqp} = \frac{V_{sc}}{I_{sc}} \angle \theta$$

$$\theta = \cos^{-1} \frac{P_{sc}}{V_{sc} I_{sc}}$$

$$R_{eqp} = \frac{V_{sc}}{I_{sc}} \cos \theta$$

$$X_{eqp} = \frac{V_{sc}}{I_{sc}} \sin \theta$$

(12)

from this test
we find copper loss

③ Dc Test


* Apply Dc Voltage to Any side of the transformer.

X $\rightarrow$ short circuit

$$Z_{in} = R_p = \frac{V_{DC}}{I_{DC}}$$

- If test on primary.

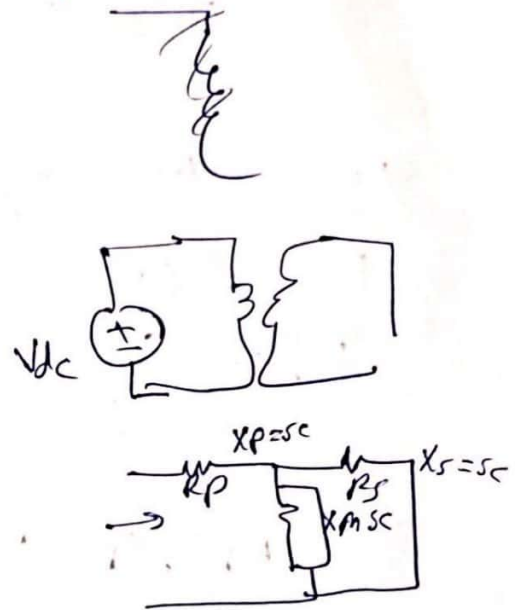- If test on secondary $R_s = \frac{V_{DC}}{I_{DC}}$ on secondary.



Example :-

VP VS

20kVA, 8000/240V, 60Hz. transformer.

The following Test taken.

$$a = \frac{V_P}{V_S} = \frac{8000}{240}$$

* open-circuit test
(on primary)

$$V_{oc} = 8000V \quad I_{oc} = 0.214A \quad P_{oc} = 4000W$$

* Short-circuit test
(on primary)

$$V_{sc} = 489V \quad I_{sc} = 2.5A \quad P_{sc} = 240W$$

from open circuit $\Rightarrow$

$$Y_{oc} = \frac{I_{oc}}{V_{oc}} \angle \theta \Rightarrow \theta = \cos^{-1} \frac{P_{oc}}{V_{oc} I_{oc}} = \cos^{-1} \frac{4000}{8000 \times 0.214} = 76.5^\circ$$

$$Y_{oc} = \frac{0.214}{8000} \angle -76.5^\circ = \frac{0.0000263}{\frac{1}{R_c}} - j \frac{0.0000261}{\frac{1}{X_m}}$$

$$Y_{oc} = \boxed{R_c = 159k\Omega} \quad \boxed{X_m = 38.4k\Omega} \text{ on primary.}$$

from short circuit test

$$Z_{sc} = \frac{V_{sc}}{I_{sc}} \angle \theta$$

$$\theta = \cos^{-1} \frac{P_{sc}}{V_{sc} I_{sc}} = 78.7^\circ$$

$$Z_{sc} = 195.6 \angle 78.7^\circ = \underbrace{38.4}_{R_{eqp}} + j \underbrace{192}_{X_{eqp}}$$

$\rightarrow$ test on primary

$$R_{eqp} = R_p + a^2 R_s$$

$$X_{eqp} = X_p + a^2 X_s$$

(19)

If test on secondary
side (short circuit test)

$$R_{eqs} = R_s + \frac{R_p}{a^2}$$

$$X_{eq} = X_s + \frac{X_p}{a^2}$$

(20)

2.4) Real Transformer:- with losses.




* losses in transformer:-

① Copper losses (I^2R): are the resistive heating losses in the primary and secondary windings of the Transformer.

$\Rightarrow R_p \rightarrow R_s \rightarrow$ winding (L_s, L_p)

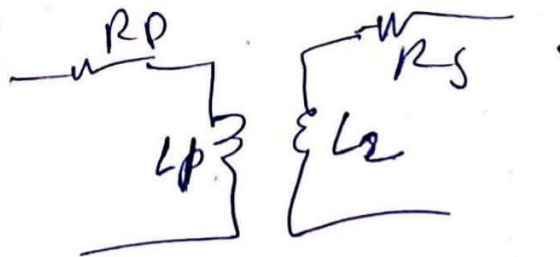
Model $\rightarrow$ Resistance R_p with primary core.
 $\rightarrow$ Resistance R_s in series with secondary coil.



(10)

1.8) Linear DC machines.

to understand DC machines.

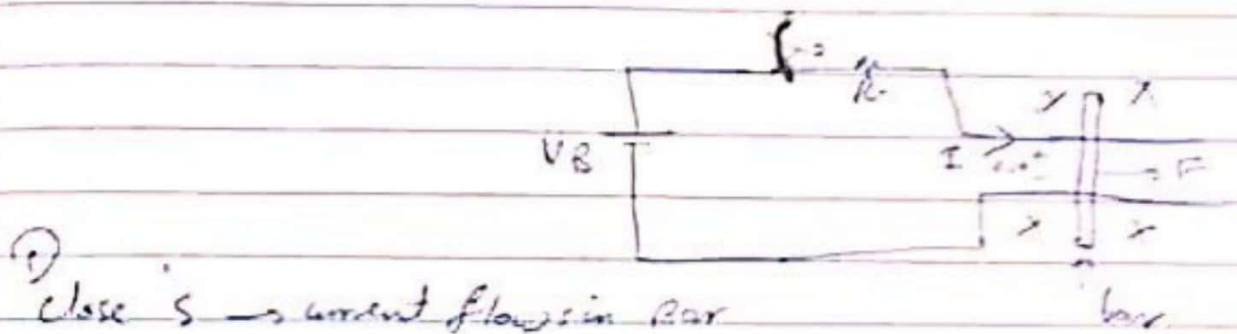

① close's → current flows in bar

$$I = \frac{V_B - e_{ind}}{R}$$

Initial $e_{ind} = 0$ $I = \frac{V_B}{R}$

② current carrying wire in presence of a field $\vec{F}$
~~Bar is not~~ Force $F = ILB$ right

Bar accelerate to right, $v \uparrow$, $e_{ind} \uparrow$
 $e_{ind} = vBL$ upward.

$$I = \frac{V_B - e_{ind}}{R} \text{ to red}$$

as $e_{ind} \uparrow \rightarrow I \downarrow$

$I \downarrow$, $F \downarrow \rightarrow F = 0$ → end of ~~ind~~

until v steady state $e_{ind} = V_B$

$$e_{ind} = V_B = vBL$$

It is a.

$I = 0$ constant no load
 speed v_{ss}

⇒ principle of motor at no load

① $i = \frac{V_B}{R}$ ② $F = ILB$ ③ $v \uparrow$ ④ $e_{ind} = vBL \uparrow$

⑤ $I \downarrow$ $F_{ind} \downarrow \rightarrow F_{ind} = 0$ $e_{ind} = V_B$

①


If an external load is added.

Opp Flow is opposite to the direction of motion

①

$$F_{\text{net}} = F_{\text{load}} - F_{\text{ind}}$$

slow the bar $v \downarrow$

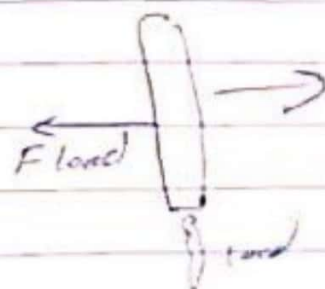

② $e_{\text{ind}} = vBL \downarrow < vB$

③ $I = \frac{vB - e_{\text{ind}}}{R} \uparrow$

④ $F_{\text{ind}} = ILB \uparrow$ until $F_{\text{ind}} = F_{\text{load}}$
steady state velocity at lower
 $v_s < v_{ss}$

electrical power $e_{\text{ind}} I$ ^{convert to} ~~lost~~ mechanical power $F_{\text{load}} v_s$
in real machines Z.W

① $F_{\text{ind}} = 0$ $F_{\text{load}} \uparrow$ applying ② $v \downarrow$ ③ $e_{\text{ind}} \downarrow$ ④ $I \uparrow$
 $F_{\text{ind}} \uparrow \rightarrow F_{\text{ind}} = F_{\text{load}}$

Motor

⑤

as a generator: - F_{applied} .

① F_{applied} is applied to the direction of motion

② $v \uparrow$

③ $e_{\text{ind}} \uparrow > V_B$ $\Rightarrow$ I $\downarrow$

(I reverse direction) I change direction

④ $F_{\text{ind}} \uparrow$ to left $\rightarrow F_{\text{ind}} = F_{\text{app}}$

$$I = \frac{e_{\text{ind}} - V_B}{R} \text{ (charge battery)}$$

mechanical power $F_{\text{ind}} v \rightarrow$ convert to $e_{\text{ind}} i$

ex

(1:10)


Generate

③

DC machines

$$e_{ind} = VBL \sin \theta$$
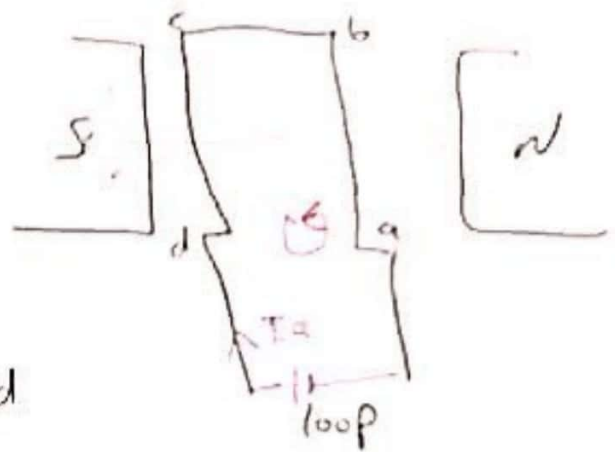
$$F \times \tau = IL \sin \theta B \sin 90^\circ$$



e_{ind} from ab, cd

$$e_{ind} = 2UBL$$

for Rotational motion

$$\omega = \frac{v}{r}$$

$$B = \frac{\Phi}{A}$$

$$e_{ind} = 2kBL$$

$$e_{ind} = 2\omega \frac{\Phi}{A} L \quad k \text{ const}$$

$$E_a = k\Phi\omega \quad \text{OR}$$

$$E = k\Phi n$$

$$\tau = kI\Phi$$


$$B = \frac{\Phi}{A}$$

$$\tau = k\Phi I$$

the most Important Equations.

$E_a \rightarrow$ AC signal

must converted to DC

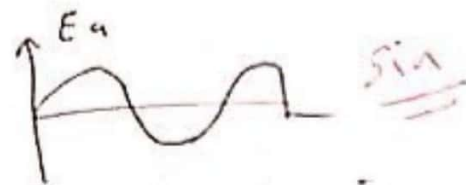

(4)


To convert output AC to DC

⇒ Commutation process


Commutation process : is the process of switching the loop connections on the rotor of a DC machine just as the voltage in the loop switches polarity, in order to maintain an essentially constant dc output voltage.

Rotating segments are attached to Rotating loop are called commutator segments (copper bars).

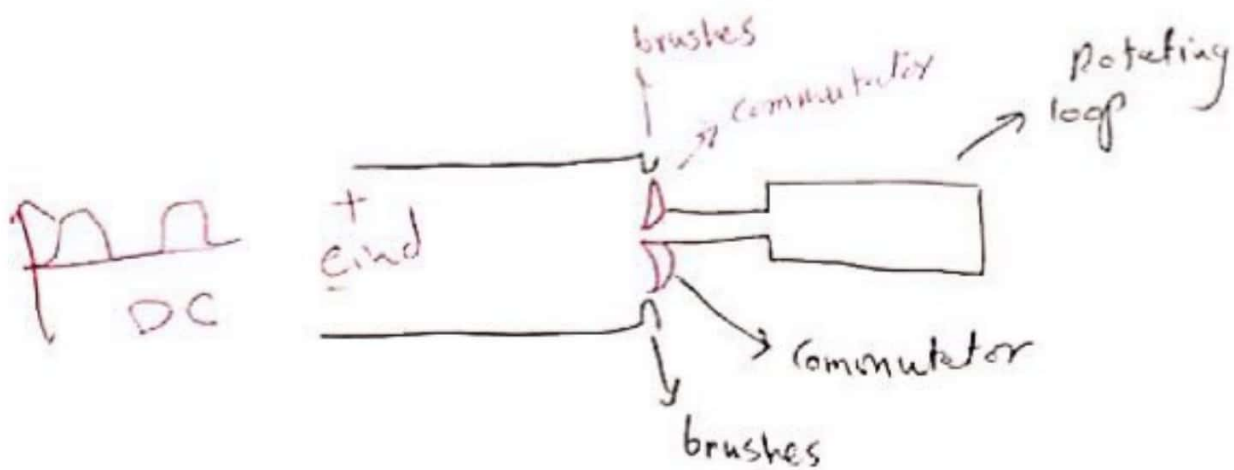Stationary pieces that ride on top of the moving segments are called brushes (graphite)



(5)

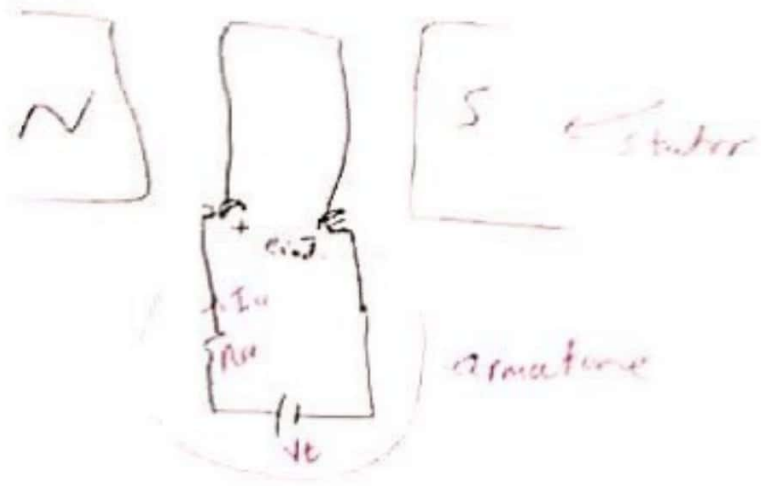

Stator : consist of field winding to produce magnetic field (field winding)
(stationary part) $\rightarrow$ circ. sp.

Rotor : Rotating part $\rightarrow$ circ. sp.
consist of armature winding (loop)

If I_a $V_t > e_{ind} \rightarrow$ Motor


If $e_{ind} > V_t \rightarrow$ Generator.

loop rotating around fixed shaft.

(6)

Chapter (8) DC Motors


equivalent circuit for DC motors

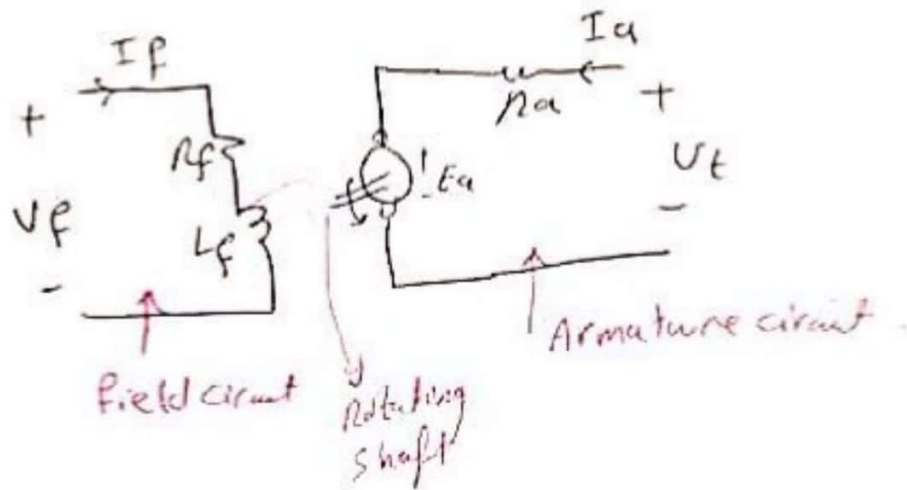

stator : consists of field winding L_f (coils)

— R_f Internal Resistance of L_f

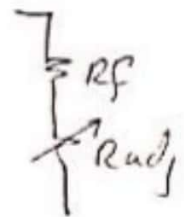R_{adj} Insert in series with R_f
for speed control.




— V_f to give $I_f \rightarrow I_f$ pass through L_f
 $\Rightarrow$ giving a magnetic field

This field effected ~~rotor~~ ^{Rotor} ~~shaft~~ with
an existing of I_a the shaft (Rotor)
Rotate around the fixed shaft

⑦


Types of Motor :-

① Separately excited motor

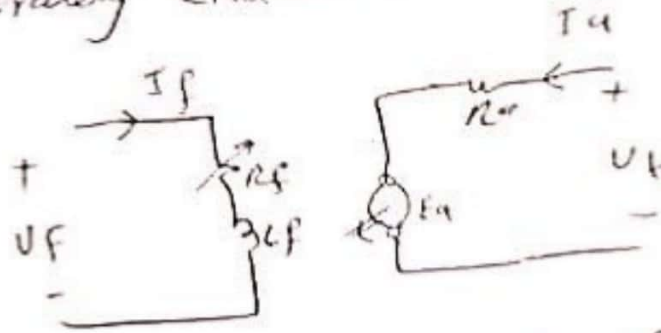


exa use two sources V_f , V_t .

② Shunt Motor

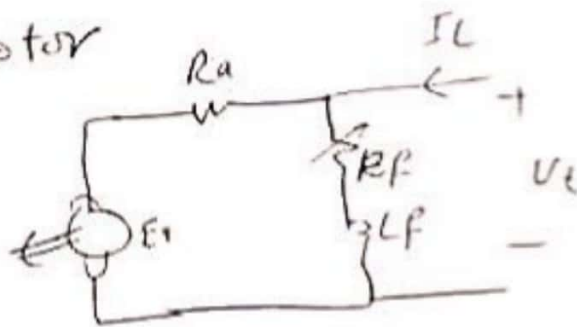

use one source (V_t) , field shunt armature.


③ series Motor

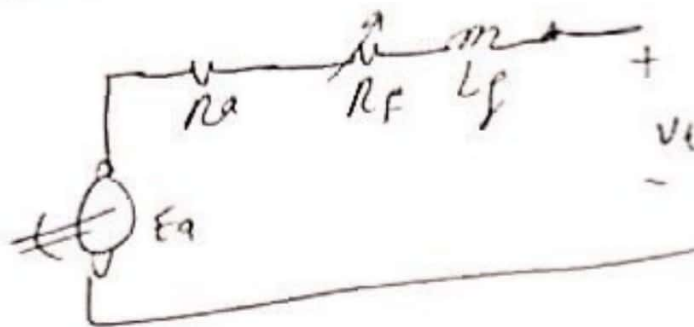


field series with Armature.

⑧

④ Compounded Motors
series + shunt field

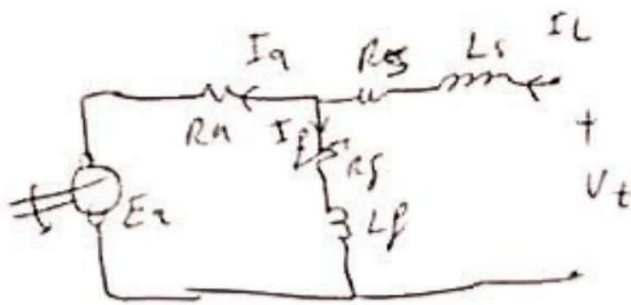


short-shunt

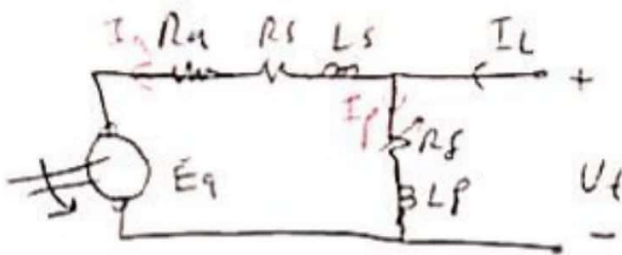

long-shunt

* Separately excited and Shunt Motor

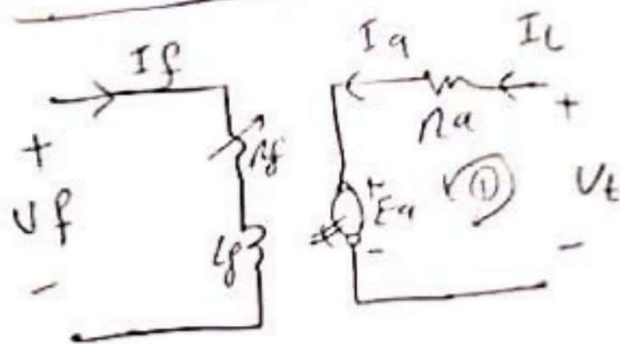

$$I_L = I_a$$

loop (1)

$$V_t = I_a R_a + E_a$$

$$I_f = \frac{V_f}{R_f}$$


$R_f \rightarrow$ shunt circuit
DC source

$$V_t = E_a + I_a R_a \quad (1)$$

for Shunt Motor

$$I_L = I_a + I_f$$

$$I_f = \frac{V_t}{R_f}$$

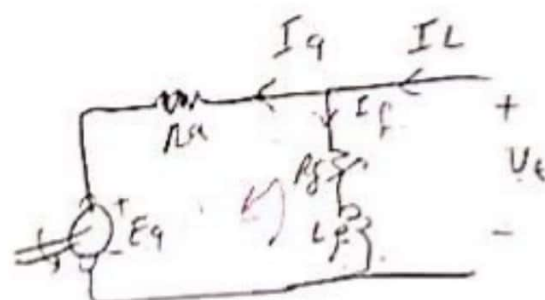


$$V_t = E_a + I_a R_a \quad (2)$$

equation (1) $\approx$ (2)

So terminal characteristic of shunt motor is the same as separately excited motor (SEM)

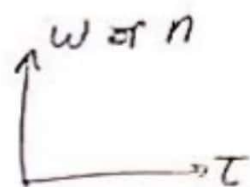Terminal characteristic for motors between speed and load (T)
To find $(\omega, T) \rightarrow$



(10)

$$V_t = E_g + I_a R_a$$

$$E_g = k \phi n \text{ or } k \phi \omega \quad (1)$$


$$\tau = k \phi I_a \quad (2)$$

$$n = \frac{60}{2\pi} \omega$$

$$V_t = k \phi \omega + \frac{\tau}{k \phi} R_a$$

$$\omega = \frac{V_t}{k \phi} - \frac{R_a}{(k \phi)^2} \tau$$

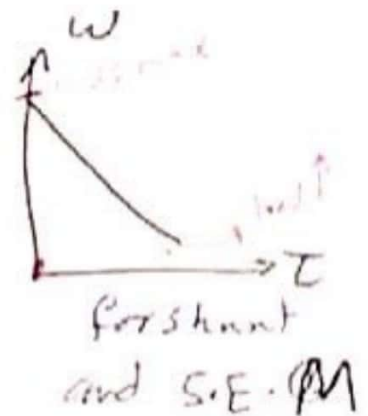at $\tau = 0$ $\omega = \frac{V_t}{k \phi}$
max speed



at $\tau = 0 \rightarrow$ no load condition

① $I_a = 0$ $\tau = k \phi I_a$

② $\tau = 0$

③ $\omega = \omega_{ss}$ max speed.

④ $V_t = E_g$


(11)

all DC machines have an armature reaction problem.

Armature reaction: with load, $I_a \uparrow$, I_a will produce a magnetic field of its own this field will distort the original magnetic field from field circuit
so total flux will decrease $\rightarrow$
weakening of the flux $\Phi \downarrow$

$$\Phi = \Phi_f - \Phi_a \downarrow$$

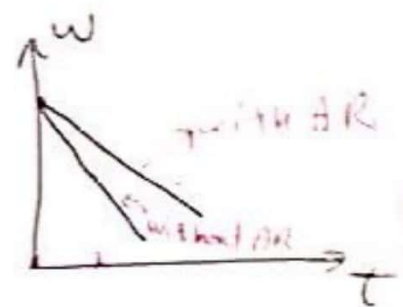if $\Phi \downarrow \rightarrow \omega \uparrow$ speed of motor will increase



AR: the distortion of the flux in DC machines occurs when the load is added to increase

$\Rightarrow$ To solve the problem $\rightarrow$ compensating winding used (CW)


(12)

using compensating winding (CW) to decrease the Armature Reaction (AR) problem.

ex 50hp, 250V, 1200rpm dc shunt motor with compensating winding. $R_a = 0.06 \Omega$, $R_{adj} + R_f = 50 \Omega$, no load speed 1200 rpm, $N_f = 1200$ Turns
 * find the speed of the motor if input current is 100, 200, 300 A
 & Find Torque.

① speed at Input current
 $I_L = 100A$
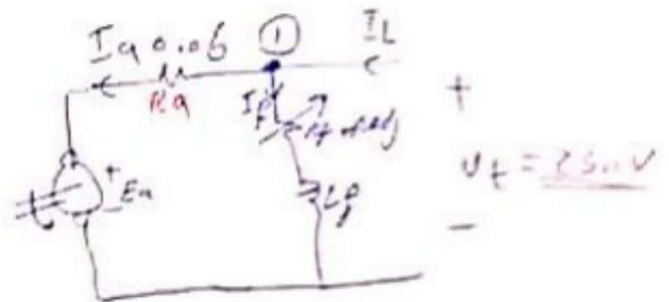
$$I_f = \frac{V_t}{R_f + R_{adj}} = \frac{250}{50} = 5A$$



$$I_a = I_L - I_f \rightarrow \text{Node ①}$$

$$= 100 - 5 = 95A$$

$$V_t = E_a + I_a R_a$$

$$E_a = V_t - I_a R_a = 250 - 95 \times 0.06 = 244.3V$$

$$E_a = 244.3 = k \Phi \omega \Rightarrow \text{speed } k \Phi ??$$

to find $k \Phi$ choose a set of values

from example no load speed = 1200 rpm

$$E_a = 250 = k \Phi 1200 \quad \text{②}$$

at no load

$$E_a = V_t = 250V$$

$$I_a = 0$$

$$I_f = 5A$$

③

$$\begin{aligned} \textcircled{1} \quad E_a &= k \phi n \\ \textcircled{2} \quad E_{a0} &= k \phi 1200 \end{aligned}$$

$$\frac{244.3}{250} = \frac{n}{1200} \rightarrow n = 1173 \text{ r/min}$$

To find torque at $I_L = 100 \text{ A}$

Power: $E_a I_a = T_{ind} \omega$

$$T_{ind} = \frac{E_a I_a}{\omega} = \frac{244.3 \times 95}{\frac{2\pi}{60} (1173)} = 190 \text{ N.m}$$

$$\omega = \frac{2\pi}{60} n$$

② Find speed, $\bar{\omega}$ at $I_L = 200 \text{ A}$

$$I_a = I_L - I_f$$

$$I_f = \frac{V_t}{R_f + R_{adj}} = 5 \text{ A}$$

$$I_a = 195 \text{ A}$$

$$E_a = V_t - I_a R_a \rightarrow E_a = 238.3 \text{ V} = k \phi n \quad \textcircled{1}$$

no load $\leftarrow E_{a0} = 250 = k \phi 1200 \quad \textcircled{2}$
 $E_{a0} = V_t = 250$

$$\frac{\textcircled{1}}{\textcircled{2}} = \frac{238.3}{250} = \frac{k \phi n}{k \phi 1200} \rightarrow n = 1144 \text{ r/min} \downarrow$$

$$T = \frac{E_a I_a}{\omega} \rightarrow T_{ind} = \frac{238.3 \times 195}{\frac{2\pi}{60} (1144)} = 388 \text{ N.m} \uparrow$$

③ speed, $\bar{\omega}$ at $I_L = 300 \text{ A}$ دکتر

$$I_a = I_L - I_f = 295 \text{ A} \rightarrow E_a = V_t - I_a R_a = 232.3 \text{ V} = k \phi n$$

$$\frac{232.3}{250} = \frac{k \phi n}{k \phi 1200} \rightarrow n = 1115 \text{ r/min} \downarrow$$

$$\bar{\omega} = \frac{E_a I_a}{\omega} = 587 \text{ N.m} \uparrow$$

if load $\uparrow$ $I_L \uparrow$ $n \downarrow$


(14) $T \uparrow$

with AR : Armature Reaction effect .

$$F_{net} = F_f - F_{AR}$$

$$N_f I_f^* = N_f I_f - F_{AR}$$

$$I_f^* = I_f - \frac{F_{AR}}{N_f}$$

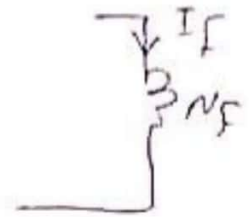

(15)

Ex 50hp, 250V, 1200r/min dc shunt motor

without compensating winding $R_a = 0.02 \Omega$

$R_f + R_{adj} = 50 \Omega$, no load speed 1200r/min, $N_F = 1200$

F of Armature Reaction $F_{AR} = 840$ A turns

If load current 200A $\rightarrow$ magnetization curve given

* Find speed if $I_L = 200$ A.

$$I_f = \frac{V_t}{R_f + R_{adj}} = \frac{250}{50} = 5A$$

$$I_a = I_L - I_f = 195A$$

$$E_a = V_t - I_a R_a$$

$$E_a = 238.3V = k \phi n \quad (1)$$

$$I_f^* = I_f - \frac{F_{AR}}{N_F} = 5 - \frac{840}{1200} = 4.3A$$

From curve $I_f^* = 4.3 \rightarrow E_{a0} = 233V$ $n_0 = 1200$ r/min

$$E_{a0} = 233 = k \phi n_0 \rightarrow 233 = k \phi 1200 \quad (2)$$

$$\frac{(1)}{(2)} = \frac{238.3}{233} = \frac{k \phi n}{k \phi 1200} \rightarrow n = 1227 \text{ r/min} \uparrow$$

$n \uparrow$ with AR

(18)

Speed control of shunt DC Motor:-

① Change R_F .

$$\text{If } R_F \uparrow \rightarrow I_F = \frac{V_t}{R_F \uparrow} \downarrow \rightarrow \text{If } I_F \downarrow$$

$$\Phi \downarrow \rightarrow E_b = k \Phi \omega \downarrow \rightarrow I_a = \frac{V_t - E_b \downarrow}{R_a} \uparrow$$

$$\text{If } I_a \uparrow \rightarrow T_{ind} = k \Phi I_a \uparrow, \text{ If } T_{ind} \uparrow$$

$$\omega \uparrow$$

$$(\text{If } R_F \uparrow \rightarrow \omega \uparrow)$$

② Change V_A (terminal voltage)

$$\text{If } V_t \uparrow \rightarrow I_a = \frac{V_t \uparrow - E_b}{R_a} \uparrow \rightarrow$$

$$\text{If } I_a \uparrow \rightarrow T_{ind} = k \Phi I_a \uparrow \rightarrow \text{If } T_{ind} \uparrow \omega$$


$$(\text{If } V_t \uparrow \rightarrow \omega \uparrow)$$

③ Insert R_{adj} in series with R_a

$$\text{If } R_a \uparrow \rightarrow I_a = \frac{V_t - E_b}{R_a \uparrow} \downarrow \rightarrow T_{ind} \downarrow \rightarrow \omega \downarrow$$


$\Rightarrow$ this method is bad because of power waste.

(17)

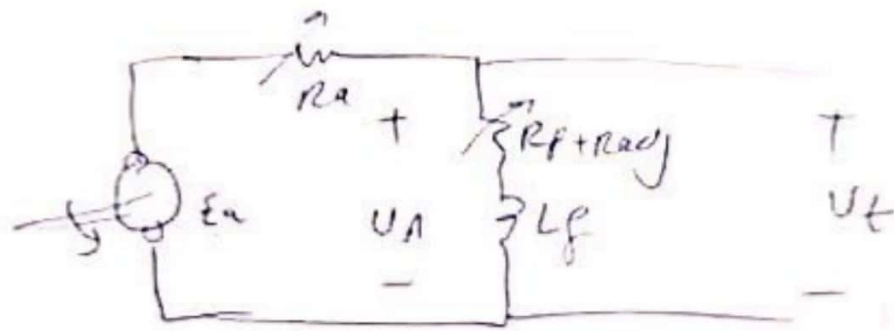

- ① change $R_f + R_{adj}$
- ② change R_a
- ③ change V_A

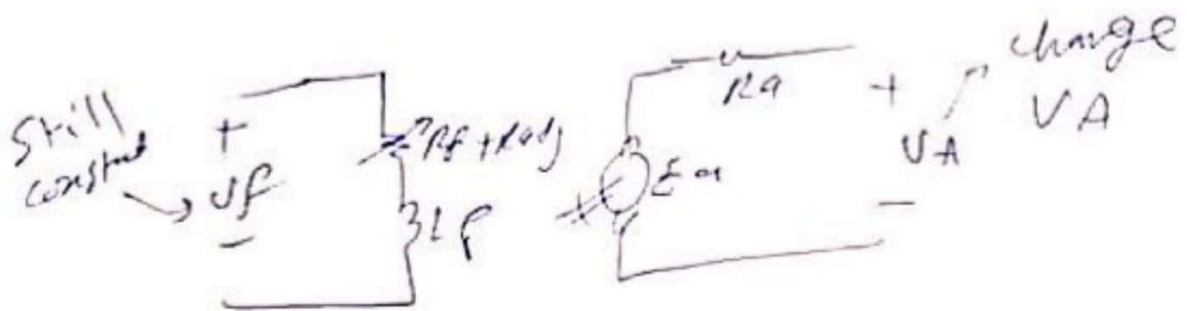To change V_A and V_E still constant
use shunt motor as separately
excited motor




(18)

* Series motor

$$I_L = I_a = I_s$$

$$V_t = E_a + I_a(R_a + R_s)$$

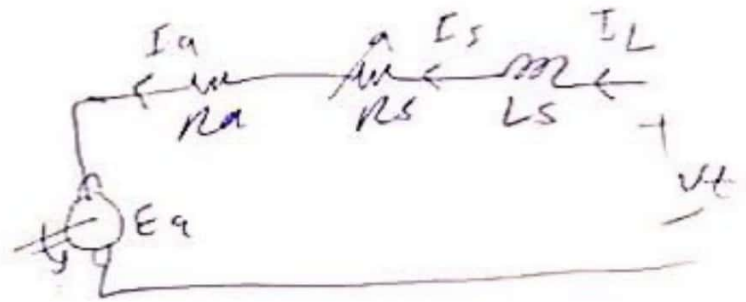

If load change $I_L = I_a = I_s$ change
 $\rightarrow$ so ϕ change

$$\phi \propto I_a \rightarrow \boxed{\phi = c I_a}$$

$$E_a = k \phi \omega \rightarrow T = k \phi I_a$$

$$\phi = c I_a$$

$$V_t = E_a + I_a(R_a + R_s)$$

$$V_t = k \phi \omega + \frac{T}{k \phi} (R_a + R_s)$$


$$\boxed{\omega = \frac{V_t}{\sqrt{k c T_{ind}}} - \frac{R_a + R_s}{k c}}$$

$$\omega \propto T_{ind}$$

at $T=0 \rightarrow$ no load

$$\boxed{\omega = \infty}$$

motor run away at
no load

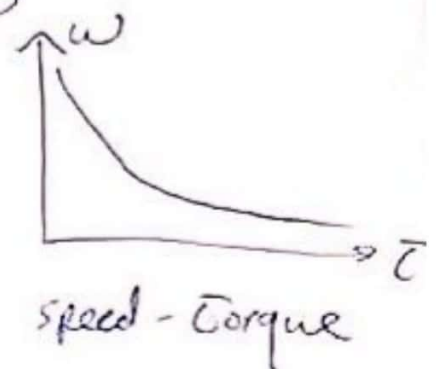

never unload series motor


series motor has higher starting torque

(19) than shunt motor.

Ex 250V, series motor, with compensating winding
 $R_A + R_S = 0.08 \Omega$, $N_S = 25$ turns.

~~$E_a = V_t - I_a$~~

find speed and Torque if $I_a = 50A$

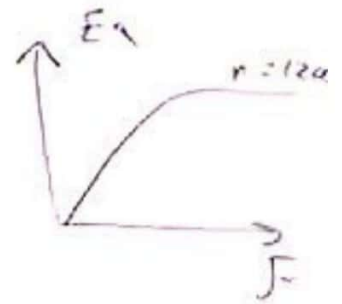

4. a $E_a = V_t - I_a(R_A + R_S)$

$$E_a = 250 - (50)(0.08) = 246V$$

$$E_a = 246 = K \Phi N \quad (1)$$

$$F = N_S I_S = N_S I_a = 1250 \text{ A} \cdot \text{turns}$$

from curve at $F = 1250 \rightarrow E_{10} = 80V$

$$80 = K \Phi (1200) \quad (2)$$

$$\frac{(1)}{(2)} = \frac{246}{80} = \frac{K \Phi n}{K \Phi 1200} \rightarrow n = 3690 \text{ r/min}$$

$$T_{ind} = \frac{E_a I_a}{\omega} = \frac{246 \times 50}{\frac{2\pi}{60} \times 3690} = \underline{\underline{31.8 \text{ Nm}}}$$

(20)

Speed control of series motor:-

① change $R_a + R_s$

$$\text{if } (R_a + R_s) \uparrow \rightarrow I_a = \frac{V_t - E_b}{R_a + R_s} \downarrow$$

$$\text{if } I_a \downarrow \rightarrow T_{ind} = k \Phi I_a \downarrow$$

$$\Rightarrow \omega \downarrow \quad (\text{waste power})$$

② change V_t

$$\text{if } V_t \uparrow \rightarrow I_a = \frac{V_t - E_b}{R_a + R_s} \uparrow$$

$$\text{if } I_a \uparrow \rightarrow T_{ind} \uparrow \rightarrow \omega \uparrow$$

②

* losses

- ① Copper loss. $(I_a^2 R_a) (I_f^2 R_f)$
- ② Brush drop loss.
- ③ Mechanical loss
- ④ core loss
- ⑤ Stray losses.

To find R_a

- ① Block Rotor so that it can't move
- ② Apply DC small voltage to Armature, change voltage until $I_a = I_{a \text{ rated}}$.


Then $R_a = \frac{V_a}{I_a}$

To find R_f

- ① supply $I_f = I_{f \text{ rated}}$.
- $$\Rightarrow R_f = \frac{V_f}{I_f}$$

Then $P_{\text{copper}} = I_a^2 R_a + I_f^2 R_f \Rightarrow \text{Copper loss}$

①

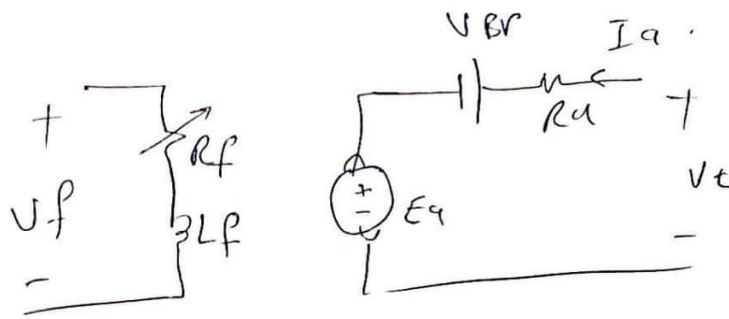

② brush loss .

$$P_{\text{brush}} = I_a V_{br}.$$

③ Rational loss at full load = Rational loss at no load .

⇒ To find $P_{\text{rational}} \rightarrow$ no load Test .
at no load $I_a \approx \text{zero}$

$$P_{\text{rational}} = P_{\text{core}} + P_{\text{mech}}.$$

OR $P_{\text{rational}} = E_g V_t I_a$ at no load test .

④ stray loss = 1% P_{in} .

P_{in} : Input power .

$$P_{in} = V_t I_L \quad \text{at full load .}$$

$$\text{efficiency} \leftarrow \eta = \frac{P_o}{P_{in}} \times 100\% = \frac{P_{in} - P_{\text{copper}} - P_{\text{rot}} - P_{\text{stray}}}{P_{in}} \times 100\%$$

②

ex 50hp, 250V, 1200 rpm DC Shunt Motor.
has a rated $I_a = 170A$, a rated field current $I_f = 5A$.
- at Rotor blocked Test: $V_A = 10.2V \rightarrow I_a = 170A$.

- $V_f = 250V \Rightarrow I_f = 5A$.

- $V_{br} = 2V$.

- At no load $V_t = 240V \rightarrow I_a = 13.2A$.
 $I_f = 4.8A$, $n = 1150 \text{ rpm}$.

* Calculate efficiency

$R_A \rightarrow$ from blocked Rotor Test.

$$R_A = \frac{V_A}{I_a} = \frac{10.2}{170} = 0.06A$$

$$R_f = \frac{250}{5} = \frac{V_f}{I_f} = 50\Omega$$

$$P_A = I_a^2 R_A = (170)^2 (0.06) = 1734W$$

$$P_f = (I_f)^2 R_f = (5)^2 (50) = 1250W$$

$$P_{brush} = V_{br} I_a = (2)(170) = 340W$$

$P_{rot} = V_t I_a$ at no load Test.

$$P_{rot} = (240)(13.2) = 3168W$$

(3)

$$P_{in} = V_T I_L$$

$$= (250)(175) = 43750 \text{ W}$$

$$P_o = P_{in} - P_{loss}$$

$$P_{loss} = P_{Gres} + P_A + P_F + P_{rot}$$

$$P_o = 36820 \text{ W}$$

$$\eta = \frac{P_o}{P_{in}} \times 100\%$$

$$\eta = \frac{36820}{43750} \times 100\% = 84.2\%$$

(4)